
 


Computational model-free active gate driver control

For SiC MOSFETs



Nart Gashi

 



So why is the monitor shutting down?

  
Answer: Bad EMC design! (Both of my 2 kW boost converter and the monitor HDMI adapter)



Switching cycles:





Switching transients:

 



**At the core of EMC-related
challenges in power converters
lies the power switching device**

**SiC MOSFET dv/dt : 200
V/ns**


Conventional gate drivers:

  

Active gate drivers:

  


 Intelligent gate-drives (closed-loop control)




Electromagnetic Interference improvement

 Fast switching in WBG devices can increase EMI, which can be suppressed through adaptive gate-voltage control.




Improving Current imbalance in multi-die packaging

 Uneven current sharing and turn-on gate-drive oscillations in SiC modules can be mitigated with intelligent gate drivers.



Device lifetime enhancement

 
Through smart control of switching and conduction losses, by minimizing thermal cycling.



Device Protection


Intelligent gate drivers can detect faults and degradation early, protecting devices through real-time gate-voltage adjustment.

 Intelligent gate-drives (closed-loop control)




Electromagnetic Interference improvement

 Fast switching in WBG devices can increase EMI, which can be suppressed through adaptive gate-voltage control.




Improving Current imbalance in multi-die packaging

 Uneven current sharing and turn-on gate-drive oscillations in SiC modules can be mitigated with intelligent gate drivers.



Device lifetime enhancement

 Through smart control of switching and conduction losses, by minimizing thermal cycling.



Device Protection

Intelligent gate drivers can detect faults and degradation early, protecting devices through real-time gate-voltage adjustment.

Challenges in intelligent gate drivers

- Switching events last only a few tens to hundreds of nanoseconds


Difficulties in sensing

- Device models are highly inaccurate and nonlinear
- Device behaviour changes through temperature change and aging
- Device behaviour is also based on the layout and converter topology


Difficulties in modelling for control

- Limited computational capabilities

Difficulties in computational
control

 

 Computational model-free active gate driver control



Topology of active gate driver (MMDAGD)


- Voltage-source based gate driver composed of series connecting l floating sub-modules V_{SM}

- A turn-on/turn-off profile (or sequence) is defined as k steps:

$$\mathbf{v} = [v_1, v_2, \dots, v_k]$$


- Where the feasible voltage construction set is defined as:
 
$$\mathcal{V} = \{0, \Delta v, 2\Delta v, \dots, (2^l - 1)\Delta v\}$$



[1]: Takayama, H., Fukunaga, S. and Hikiyama, T., 2023, September. Binary-weighted modular multi-level digital active gate driver. In 2023 25th European Conference on Power Electronics and Applications (EPE'23 ECCE Europe) (pp. 1-8). IEEE.

 Computational model-free active gate driver control



Feedback: Peak detector


- To assess the switching performance, we utilize peak detectors to measure overshoot on
- Measuring I_{DS} (during turn-on), and/or V_{DS} (during turn-off)

- The current charging capacitor C_{pk} can be denoted as:


$$i_C(t) = I_{pk}(t) = \begin{cases} C_{pk} \frac{dv_{in}(t)}{dt}, & v_{in}(t) > v_{pk}(t) + v_{d,th}, \\ 0, & \text{otherwise.} \end{cases}$$

- In which the final (peak) voltage is denoted as:
 
$$v_{pk}(t) = v_{pk}(0) + \frac{1}{C_{pk}} \int_0^t i_C(\tau) d\tau.$$




Simplified peak detector circuit

 


Peak detector example using Vds

 Computational model-free active gate driver control



- How can we choose $v_i \in \mathcal{V}$, such that we minimize overshoot while maintaining low switching loss?

 - For switching energy losses keep the switching event as short as possible (e.g. 20 ns, 3 steps)
- For minimizing overshoot and ringing, we will optimize in real-time
- N-dimensional problem with implicit formulation, with up to $\sim 15^6$ possible solutions



- A turn-on/turn-off profile (or sequence) is defined as k steps: $\mathbf{v} = [v_1, v_2, \dots, v_k]$

MMDAGD feasible set:

$$\mathcal{V} = \{0, \Delta v, 2\Delta v, \dots, (2^l - 1)\Delta v\}$$



- Optimization objective function:

$$\mathbf{v}^* = \arg \min_{\mathbf{v} \in \mathbb{R}^k} f(\mathbf{v}) \quad \text{s.t.} \quad v_i \in \mathcal{V} \quad \forall i = 1, \dots, k.$$

- $f(\mathbf{v})$: The cost (or loss) function
- $\mathbf{v}^*$: Optimal solution

The waveform optimization algorithm: Loss (cost) function

  - Because we do not have any model, we must experiment with different waveforms in order to compute a 'loss' (or cost)
- Hence, we define $f(\mathbf{v})$ as an experiment of one or multiple switching cycles in the operating converter
- Physically, $f(\mathbf{v})$ is the averaged output voltage of the peak detector (over one or multiple switching cycles).



Waveform optimization algorithm 1 / 2 (Coordinate descent)

Coordinate descent algorithm:




- Step 1) Initialize waveform randomly
- Step 2) Start by increasing the last element in the positive direction by Δv

$$f(v_1, \dots, v_i + \Delta v, \dots, v_k) < f(v_1, \dots, v_i, \dots, v_k)$$

- Step 3) If loss improved continue until no further improvement; If not improved, probe negative direction

$$f(v_1, \dots, v_i - \Delta v, \dots, v_k) < f(v_1, \dots, v_i, \dots, v_k)$$

   - Step 4) Continue until no longer improves; Repeat same for all $v_i \in \mathbf{v}$



Waveform optimization algorithm 2 / 2 (Gradient descent)

- Step 1) Initialize waveform randomly
- Step 2) Create a ‘neighbourhood’ of candidate waveforms and evaluate all of them


$$\mathcal{N}(\mathbf{v}) = \left\{ \mathbf{v}' \in \mathbb{R}^k \mid v'_i \in \{v_i - \Delta v, v_i, v_i + \Delta v\}, \right. \\ \left. v_i \in \mathcal{V}, \forall i \in \{1, \dots, k\} \right\}.$$

- Step 3) Pick the one which yields the lowest loss


$$\mathbf{v}^{(t+1)} = \arg \min_{\mathbf{v}' \in \mathcal{N}(\mathbf{v}^{(t)})} f(\mathbf{v}').$$

- Step 4) Repeat iteratively, until a local minimum is reached:
 
$$f(\mathbf{v}^{(t+1)}) \geq f(\mathbf{v}^{(t)})$$




 The waveform optimization algorithm: Full picture




Hardware realization

 
The optimization algorithm runs on the CPU! FPGA is used to drive MMDAGD



Hardware realization

 


Front side

 


Back
side

Peak detector realization

 



Hardware realization: MMDAGD

 



- 4-level MMDAGD prototype
- MMDAGD prototype by dr. Hajime Takayama

[1]: Takayama, H., Fukunaga, S. and Hikiyara, T., 2023, September. Binary-weighted modular multi-level digital active gate driver. In 2023 25th European Conference on Power Electronics and Applications (EPE'23 ECCE Europe) (pp. 1-8). IEEE.

Double pulse test configuration

  


Boost configuration

  



Experiment configuration:

- Coordinate descent as optimizer
- Maximum regret threshold 0.8
- $V_{dc} = 80V$
- $I_{ds} \sim 40 A$ ($T_1=400 \mu s$, $T_2=T_3=20 \mu s$)
- 3 steps
- Step-duration: 30 ns

Double pulse test configuration

 

11 2 3 10.0V/ 4 5.00V/ 40

  

DC 50.0:1
DC 1.00:1

Cursors

ΔX : +2.000000us
 $1/\Delta X$: +500.00kHz
 $\Delta Y(1)$: 200.7500

00:00:09:23

Power converter settings:

- $V_{DC} \approx 35V$
- $D = 0.5$
- $V_o \approx 70V$
- $P_o \approx 125 W$
- $F_{sw} = 10 kHz$



MMDAGD Settings:

- $k = 4$ steps
- Step-duration: 20 ns

Algorithm settings:

- Max. regret = 1
- Coordinate-descent opt.

Boost configuration

  

1 50.0V/ 2 5.00A/ 3 10.0V/ 4 1.00V/

-250.0%

100.0%/

Trig'd

5

3

3

V_{gs}

V_{ds}

I_{ds}

I_L

00:00:09:02

KEYSI
TECHNOL

Acquisition

Normal

1.00GSa/s

Channels

DC 50.0

DC 10.0

DC 50.0

DC 1.00

Measurements

Top(2):

Low signal

Avg - FS(2):

5.22A

Avg - FS(3):

7.14V

Freq(3):

Power converter settings:

- $V_{DC} \approx 40V$
- $D = 0.5$
- $V_o \approx 80V$
- $P_o \approx 150 W$
- $F_{sw} = 20 kHz$



MMDAGD Settings:

- $k = 3$ steps
- Step-duration: 30 ns

Algorithm settings:

- Max. regret = 1
- Gradient descent

Boost configuration

  



Power converter settings:

- $V_{DC} \approx 40V$
- $D = 0.5$
- $V_o \approx 80V$
- $F_{sw} = 10\text{ kHz}$

MMDAGD Settings:

- $k = 3\text{ steps}$
- Step-duration: 30 ns



Algorithm settings:

- Max. regret = 2
- Coordinate descent

Experiment sequence:

Increase the load such that current flowing through inductor goes from 2.5A to 3.5A

Boost configuration

  



Experiment configuration

Power converter settings:

- $V_{DC} \approx 40V$
- $D = 0.5$
- $V_o \approx 80V$
- $F_{sw} = 10\text{ kHz}$

MMDAGD Settings:

- $k = 3\text{ steps}$
- Step-duration: 30 ns



Algorithm settings:

- Max. regret = 1
- Coordinate descent

Experiment sequence:

Heat the device from room temperature (24°C to 105°C), while operating as a boost converter, to observe how the online adaptive gate driver reacts.

Boost configuration

  



Now lets apply optimized Vgs profile to my converter (at 200V output)



Thank you for your attention!

Nart Gashi (n.gashi@tue.nl)

Under supervision of:

dr. Chengmin Li, (TU/e)

prof.dr. George Papafotiou (TU/e)

dr. Hajime Takayama (Kyoto University)