

Ki Cordless kitchen

Power Transmitter & Reference Design

Will Ettes
Intellectual Property & Standards
Philips Drachten & Eindhoven
The Netherlands

24 - 05 - 2026

innovation ✨ you



1. Introduction

- WPC organization
- Ki Cordless kitchen proposition
- Hob versus hidden transmitter case
- Ki specifications & boundaries
- Example re-worked kitchen appliance

2. Ki power chain in more detail

- From AC to DC and from DC to AC - Resistive loads
- From AC to DC, from DC to AC and from AC to DC - Motor loads
- Transmitter & Receiver power coil & NFC antenna (example)
- Z - distance vs. alignment vs. appliance footprint
- Transmitter & Receiver implementations

3. Power Control

- General Induction Hobs vs. Ki Cordless kitchen
- Duty Cycle control & Frequency control
- Burst Mode control & Duty Cycle control


4. AC analysis

- CLLC network
- First harmonic approximation
- Bode plot Induction Hob vs. Ki Cooktop case
- Bode plot Ki Cooktop vs. Concealed case for $K = 0.7$ and $K = 0.34$
- Power step response (measured)

5. Conclusion

Introduction

WPC organization

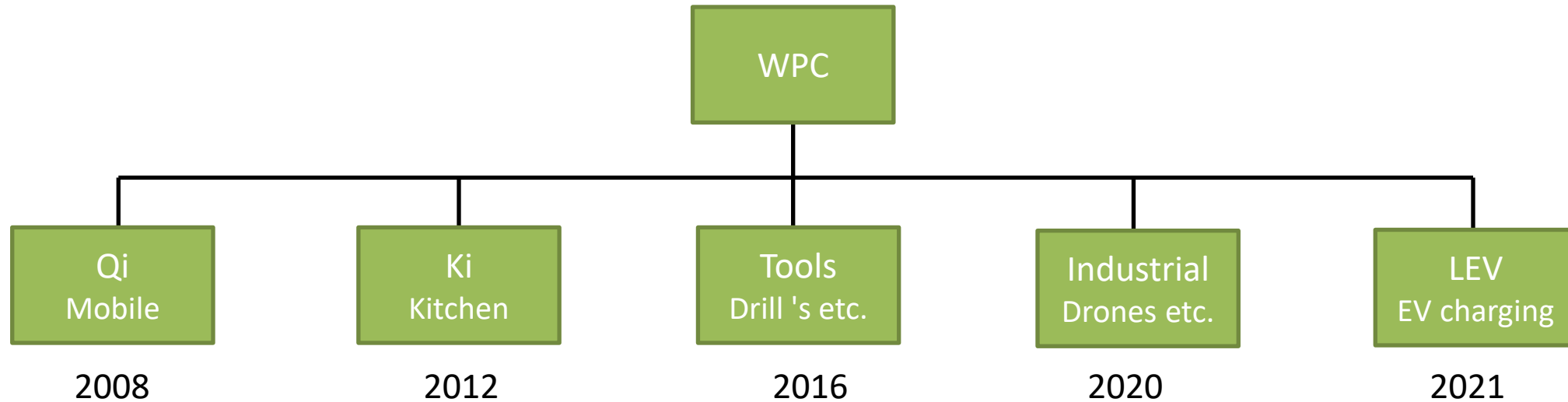

The Wireless Power Consortium (WPC) consists of a group of companies that voluntarily explores the possibilities of global standardization of wireless power technology

E.G.O., ST Micro Electronics, Midea, BSH, Philips, Group SEB (WMF), SEF, Electrolux,....


Introduction

Ki Cordless kitchen proposition



Ki power transmitter

Ki Cordless kitchen Appliance

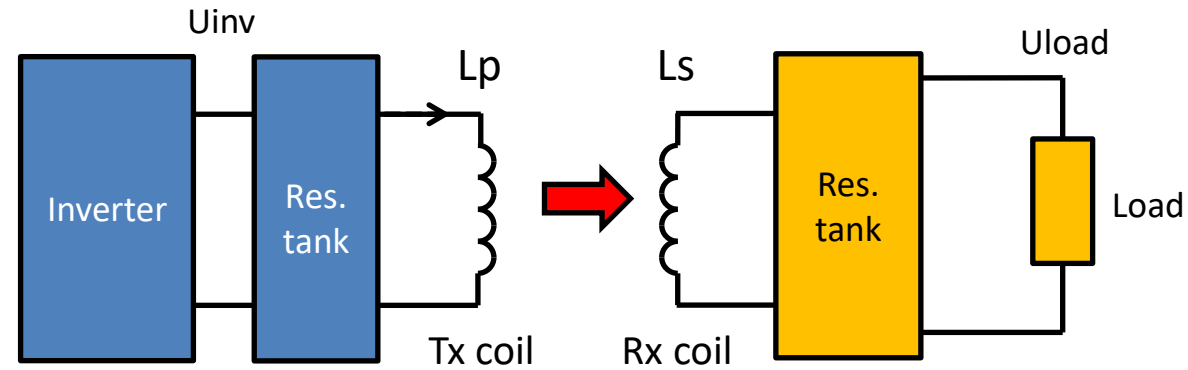

V1: Cooktop case



V2: Concealed case




Introduction

Ki specifications & boundaries

Ki power transmitter

Ki Cordless kitchen Appliance

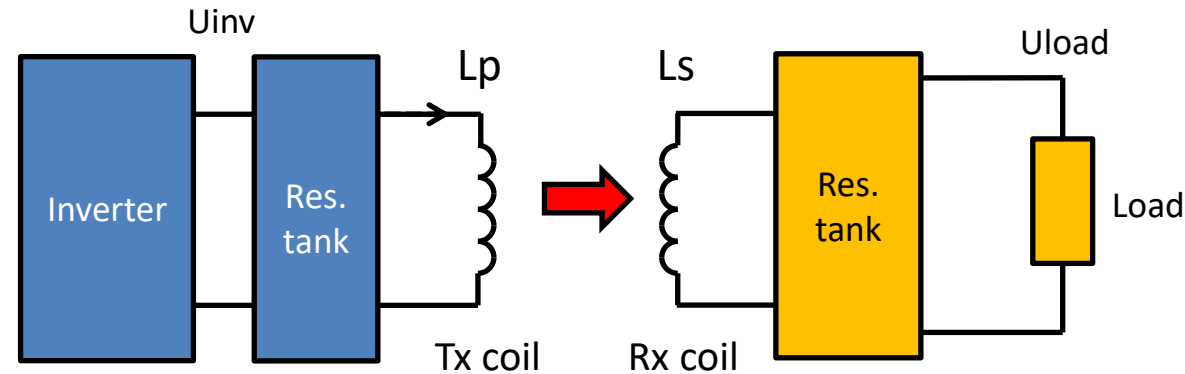

The Ki Standard should enable to power appliances:

- from 0 W to 2.2 kW
- At a frequency of 20 – 74 kHz
- At a maximum Coil – 2 – Coil distance of:
 - 1.5 cm for the hob case
 - 3.2 cm for the hidden case
- with an appliance footprint of 8 cm to 24 cm

Introduction

Example re-worked kitchen appliance



HR7778
Food processor



800 Watt
220 - 240V AC / 50Hz




Ki Power chain in more detail

From AC to DC -> DC to AC

Ki power transmitter

Ki Cordless kitchen Appliance

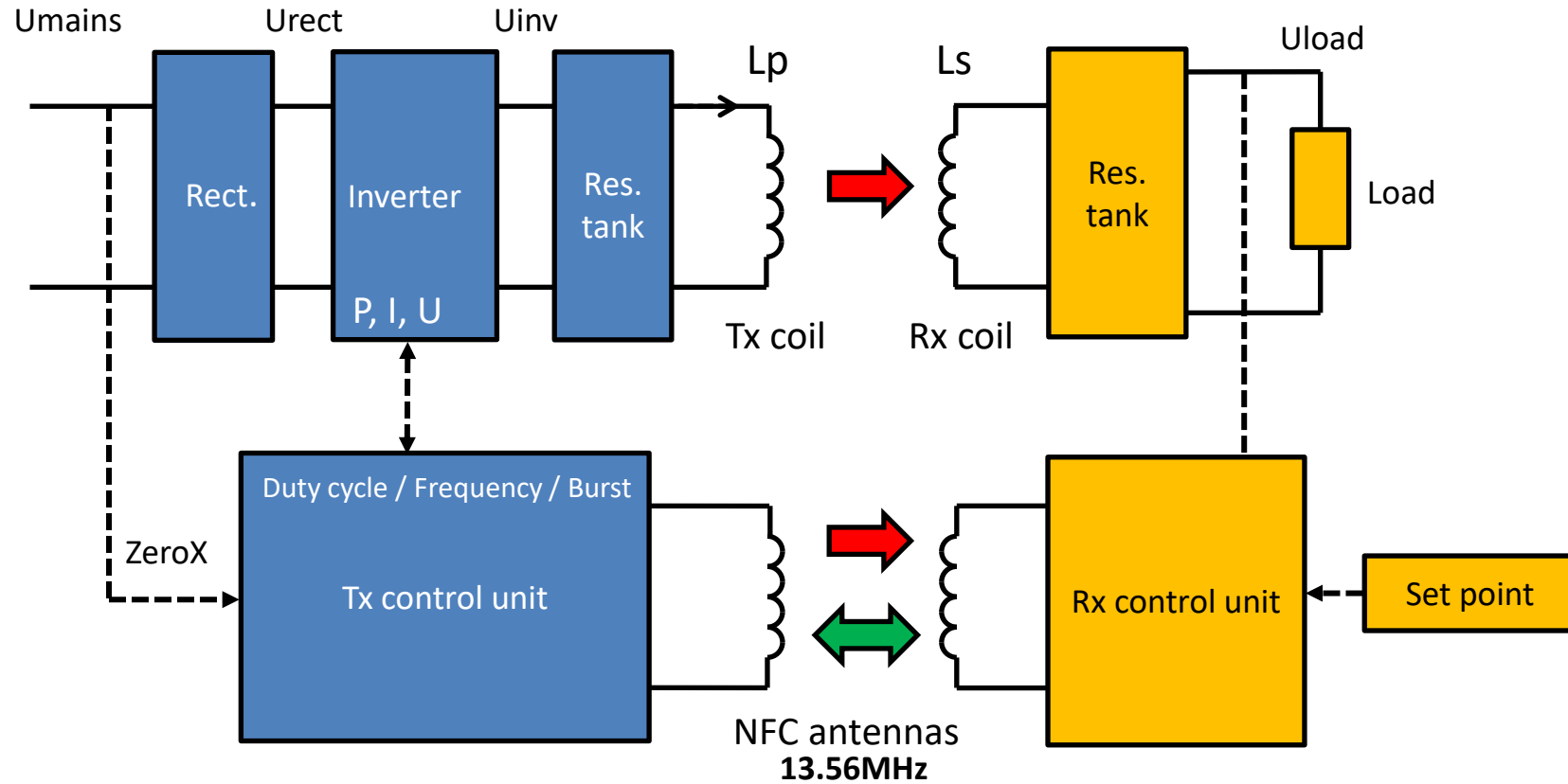

Uni-directional power channel

Bi-directional communication channel




Ki Power chain in more detail

From AC to DC -> DC to AC -> AC to DC

Ki power transmitter


Ki Cordless kitchen Appliance

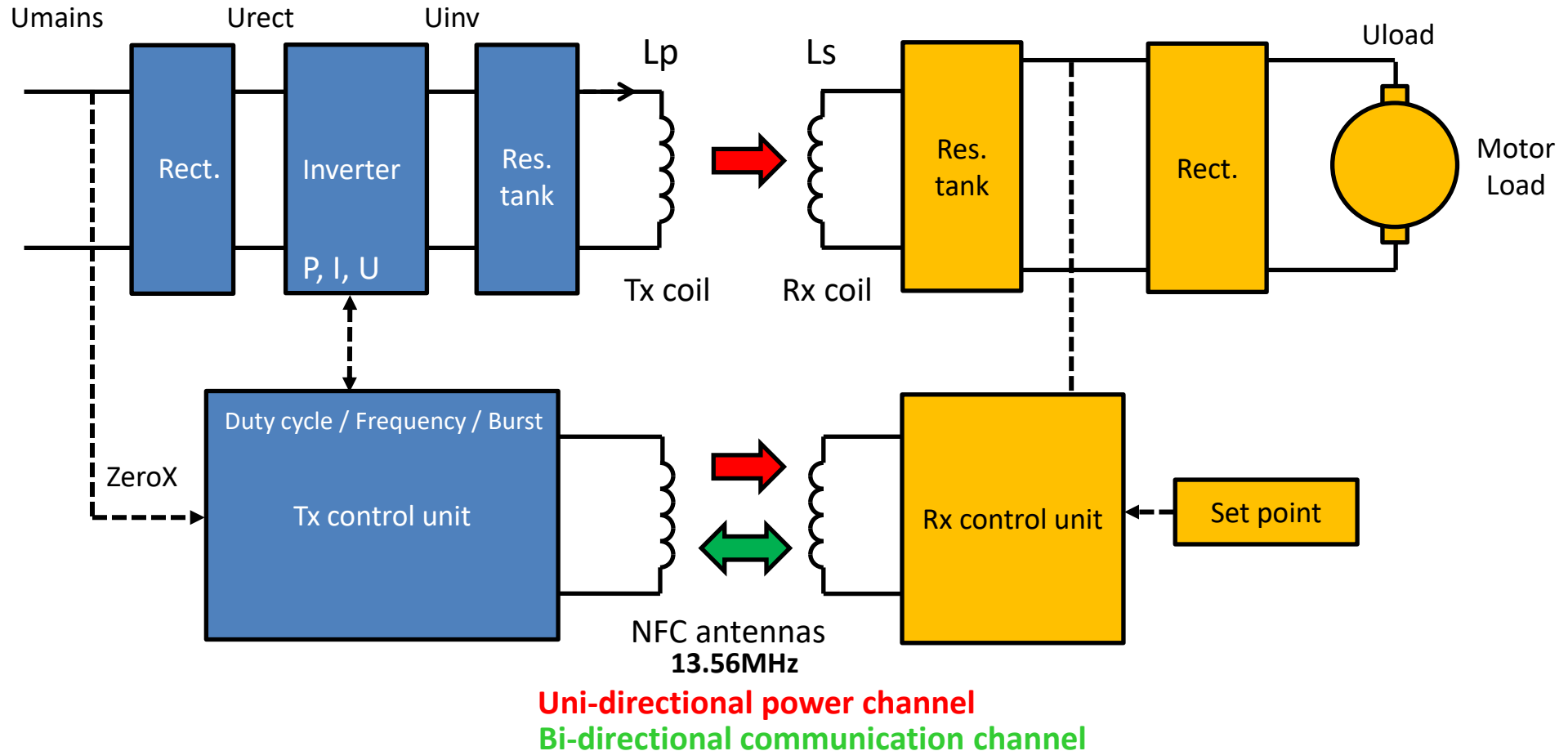



Ki Power chain in more detail

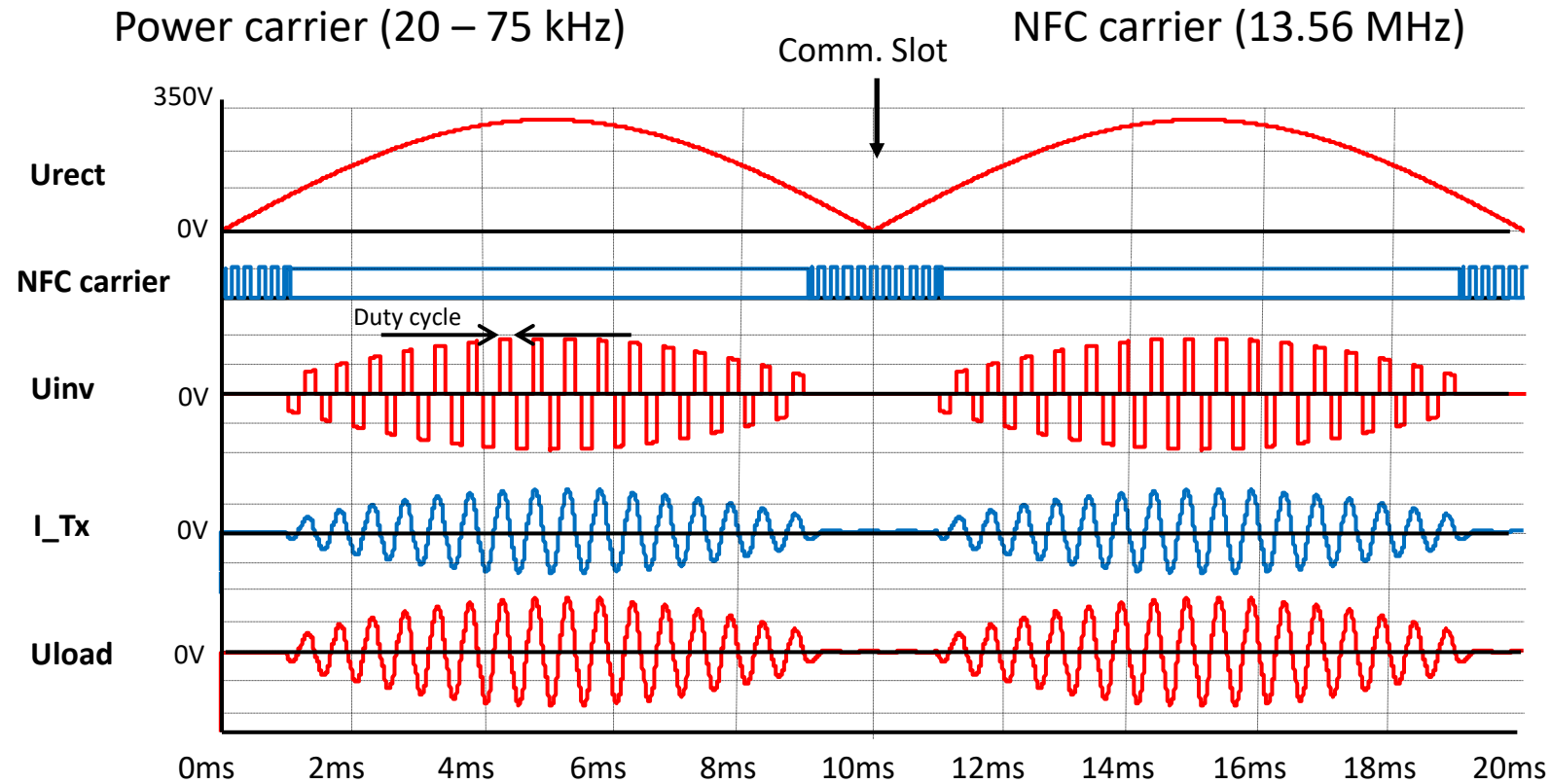
Transmitter & Receiver voltage & current wave forms




- Inverter output voltage U_{ac_HF} is shaped according the rectified mains voltage
- Communication time-slot repeats typically **20 ms** (every other zero crossing)

Ki Power chain in more detail

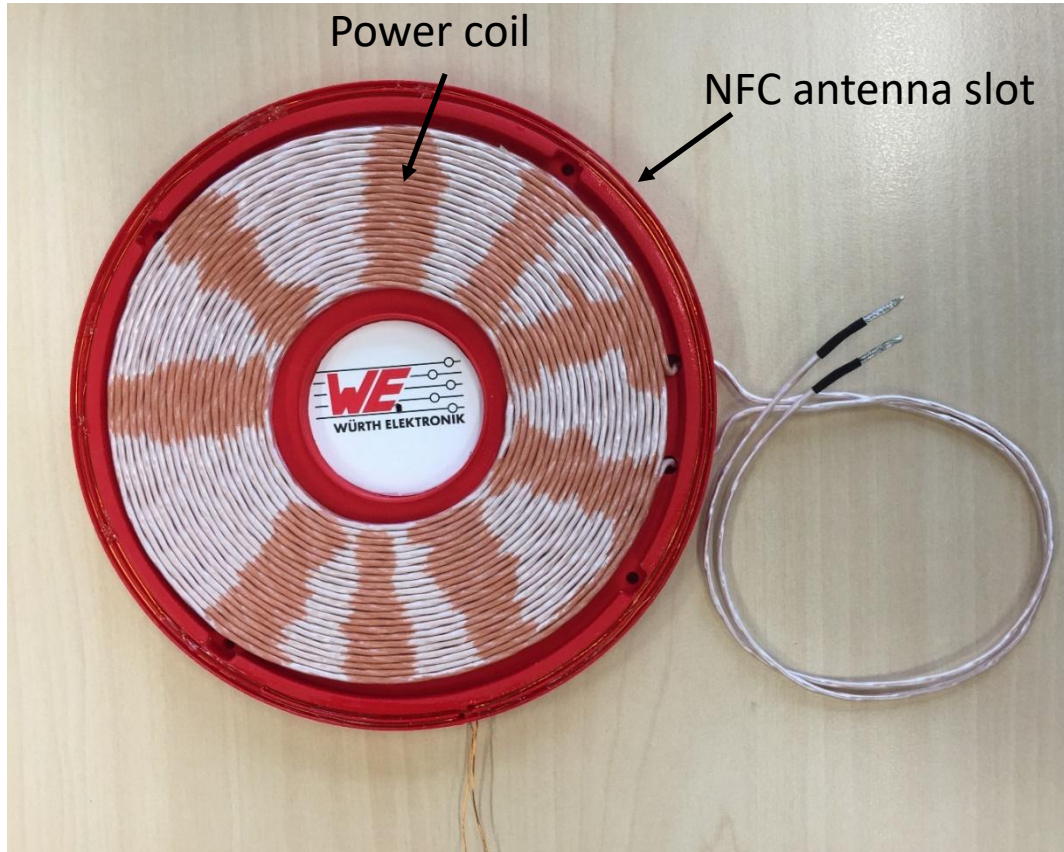Receiver power coil & NFC antenna (example from Wurth)




NFC antenna

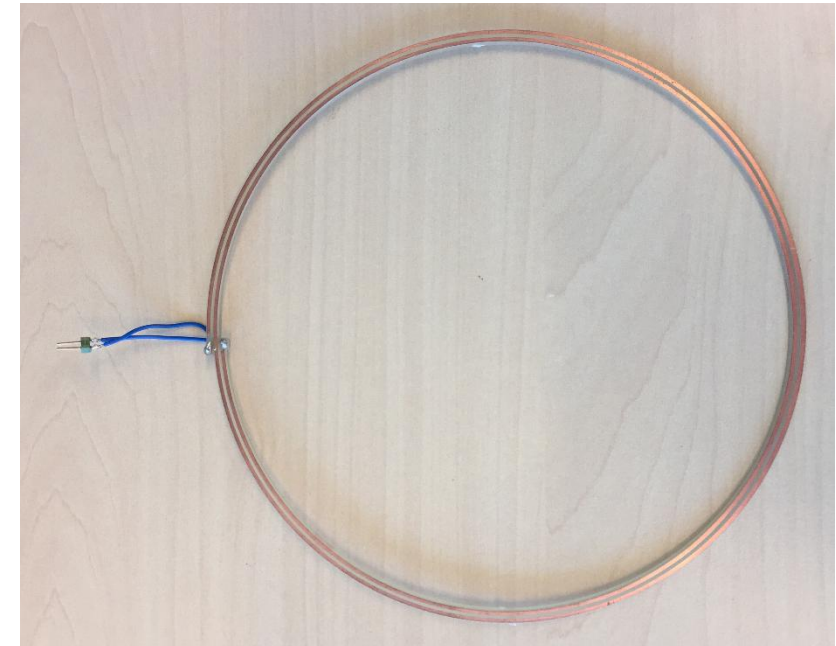

Ki Power chain in more detail

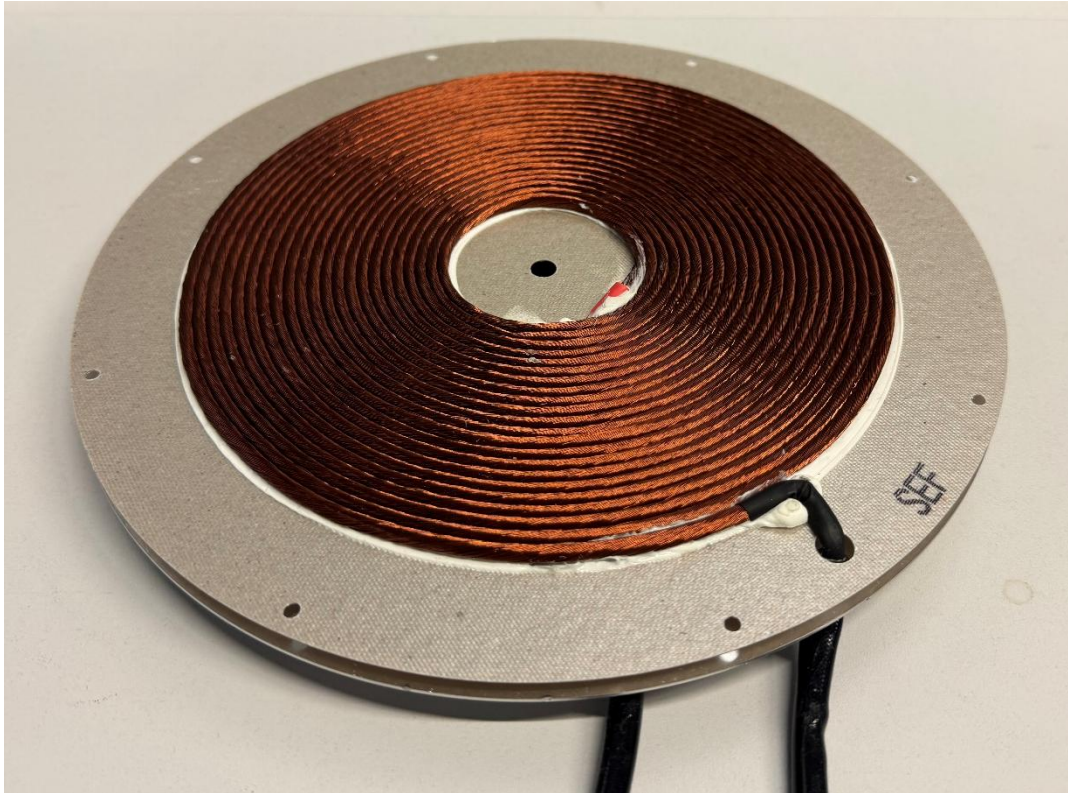
Transmitter power coil & NFC antenna (example from SEF)



With NFC antenna


Ki Power chain in more detail

Z - distance vs. alignment vs. footprint

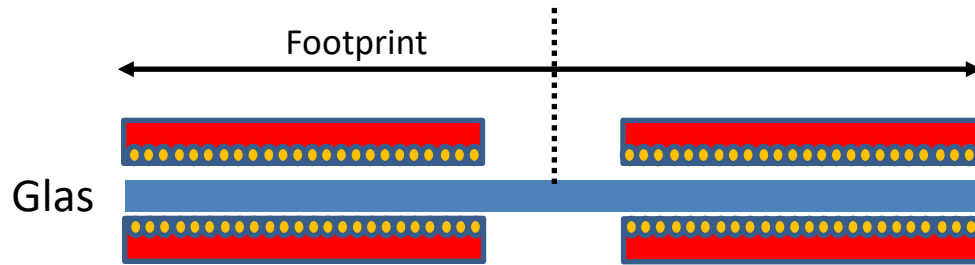

Cooktop case

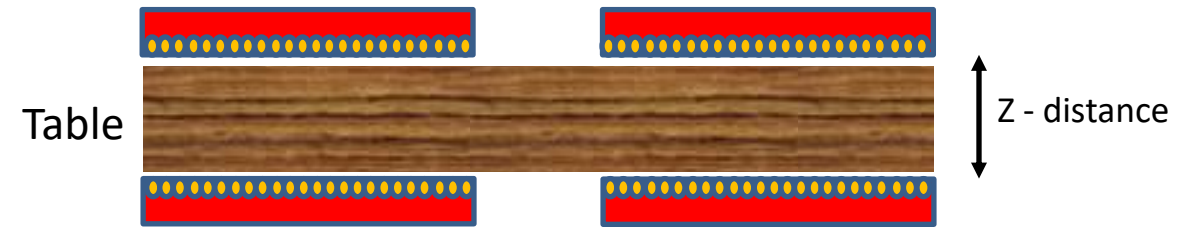Z – distance: 15mm max
K- factor range: 0.50 – 0.71



Concealed case

Z – distance: 32 mm max
K- factor range: 0.25 – 0.45

K-factor determined by:


- Z - distance
- Misalignment of the appliance
- Diameter of the Tx coil
- Footprint of the appliance

The Ki cordless appliance should be designed to operate on both platforms !




Ki Power chain in more detail

Z - distance vs. alignment vs. footprint

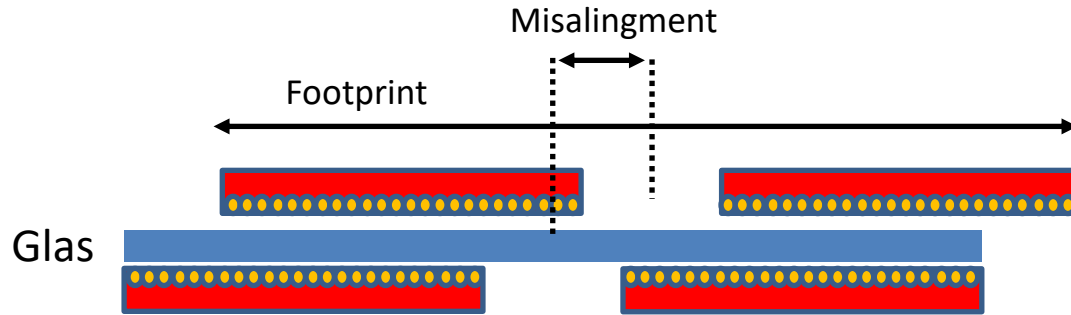

Cooktop case

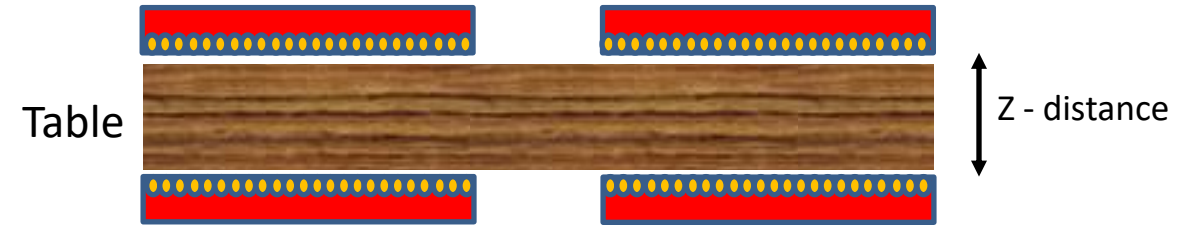Z – distance: 15mm max
K- factor range: 0.50 – 0.71



Concealed case

Z – distance: 32 mm max
K- factor range: 0.25 – 0.45

K-factor determined by:


- Z - distance
- Misalignment of the appliance
- Diameter of the Tx coil
- Footprint of the appliance

The Ki cordless appliance should be designed to operate on both platforms !




Ki Power chain in more detail

Z - distance vs. alignment vs. footprint

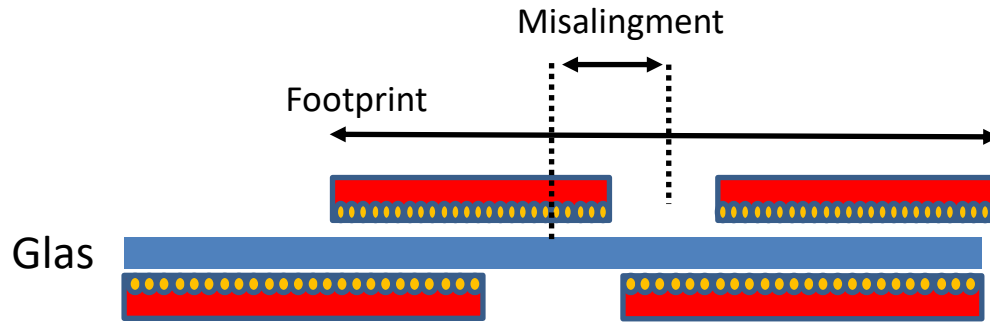

Cooktop case

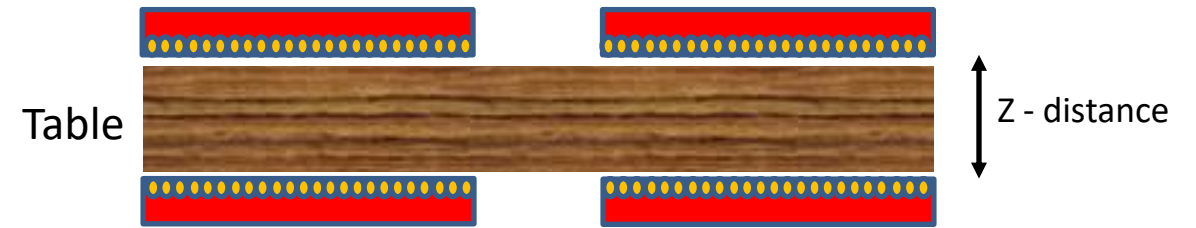Z – distance: 15mm max
K- factor range: 0.50 – 0.71



Concealed case

Z – distance: 32 mm max
K- factor range: 0.25 – 0.45

K-factor determined by:


- Z - distance
- Misalignment of the appliance
- Diameter of the Tx coil
- Footprint of the appliance

The Ki cordless appliance should be designed to operate on both platforms !



Ki Power chain in more detail

Transmitter implementation – Half bridge

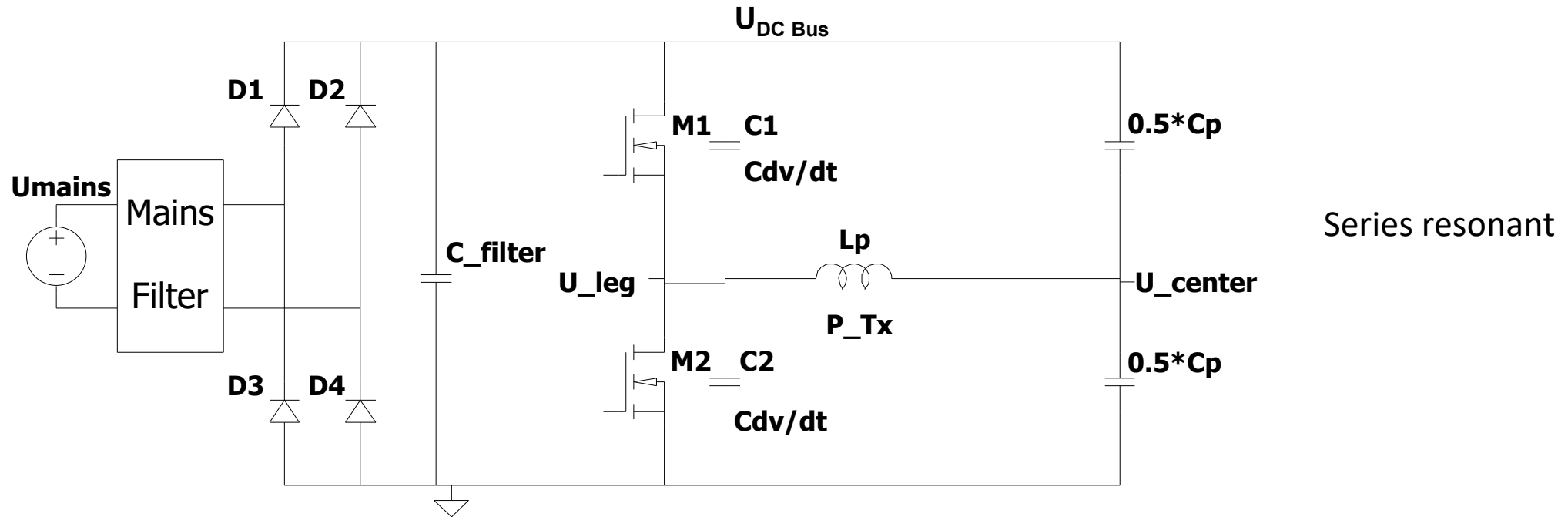

Topology of choice was driven by Induction Hob industry

- Price vs. Complexity
- Near zero power transfer difficult but possible (Duty cycle, Frequency and Burst control)


But if you can do it with a Half bridge, you can also do it with a full bridge !!

- 110 V area's -> Full bridge



Ki Power chain in more detail

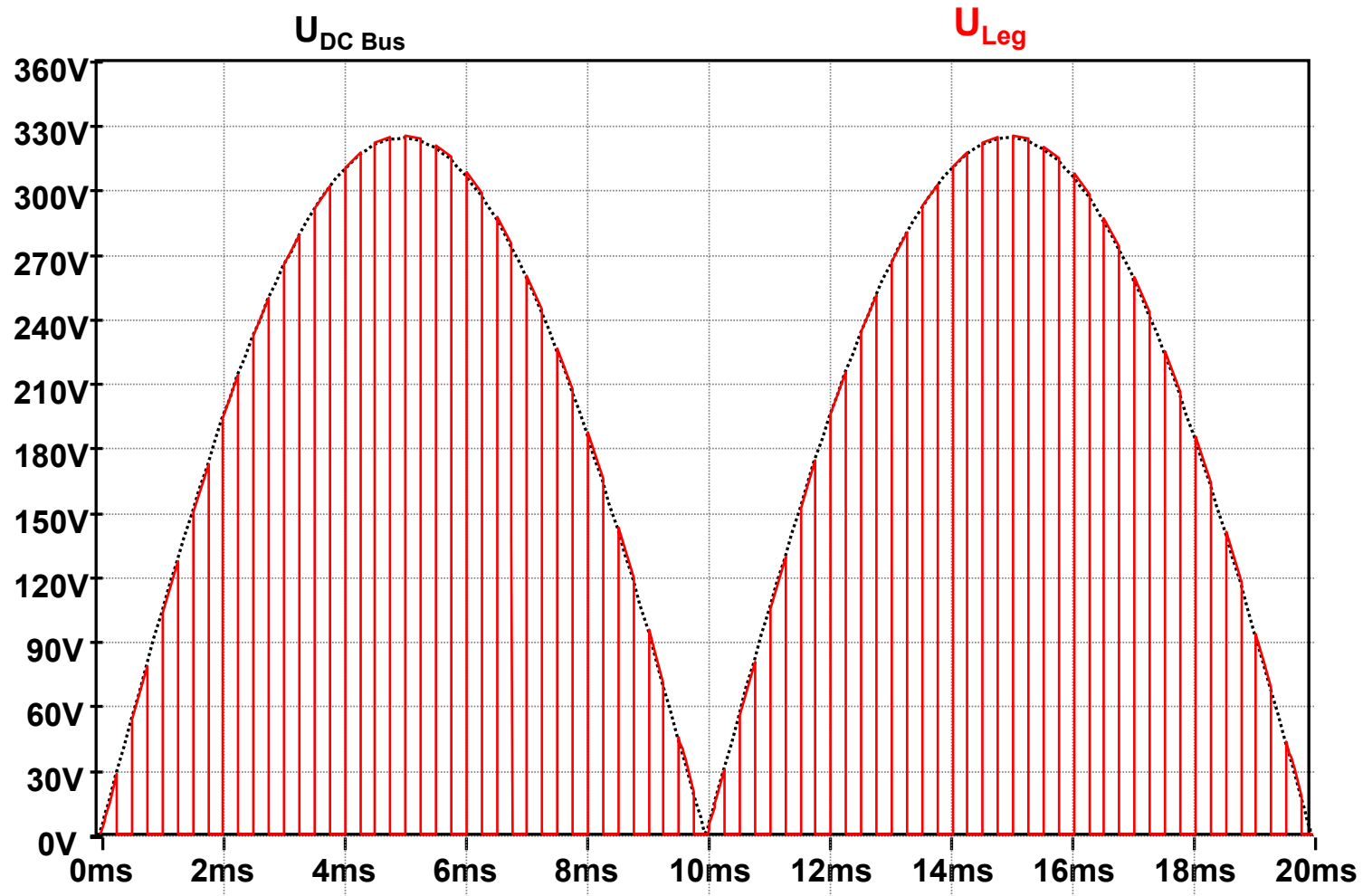$U_{DC\ Bus}$ (dotted black) and U_{Leg} (solid red) for induction hobs




$F_{Operation} = 20 - 74\text{ kHz}$


$Duty\ Cycle = 0.2 - 0.5$

Ki Power chain in more detail

Receiver implementations

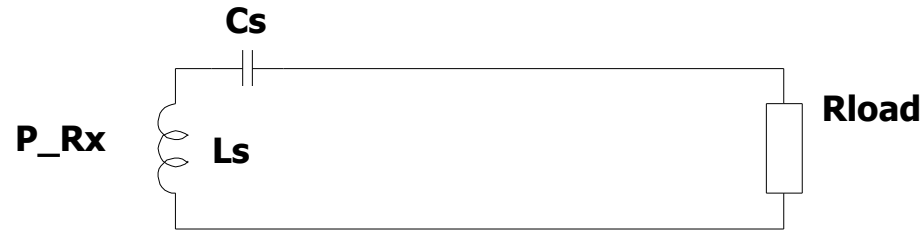

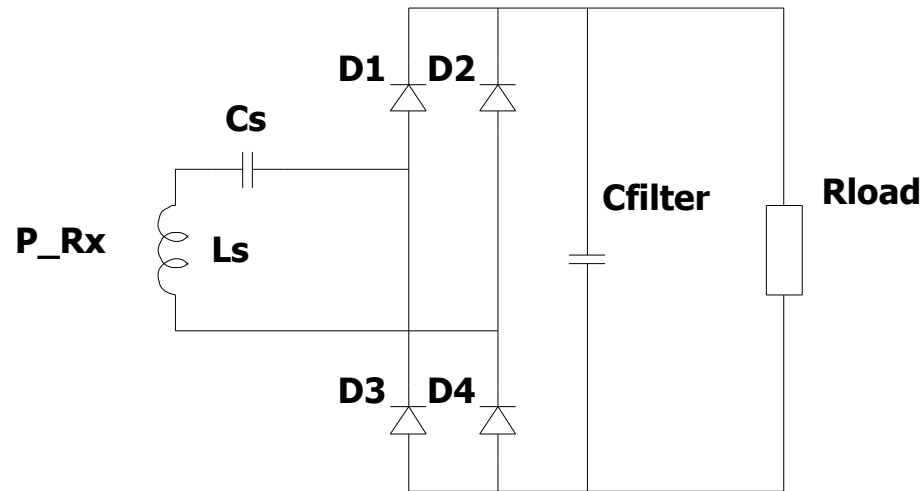
- For simple appliances like water kettles, heating elements etc.



- For appliances with:
 - motors
 - both motors & heating element


Power Control for general induction hobs

Single power control loop

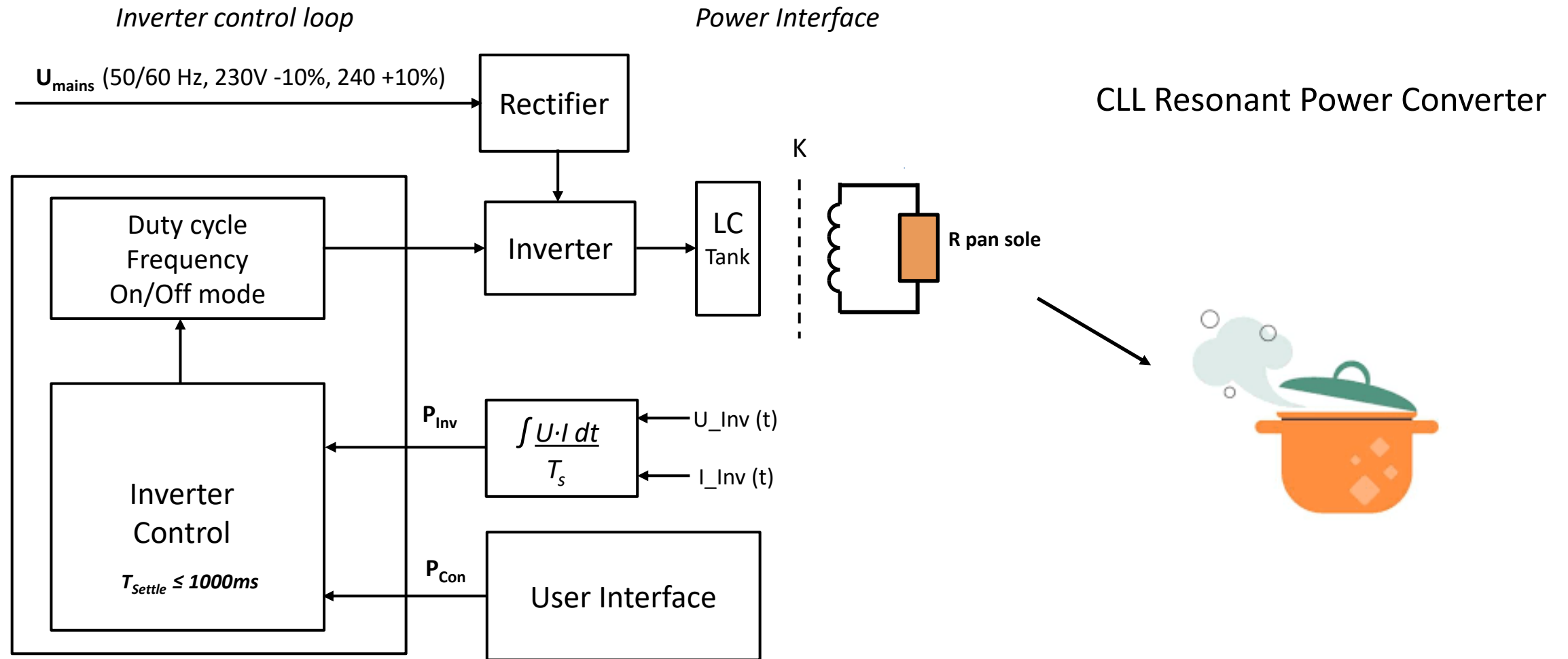


Power Control for Ki cordless kitchen system

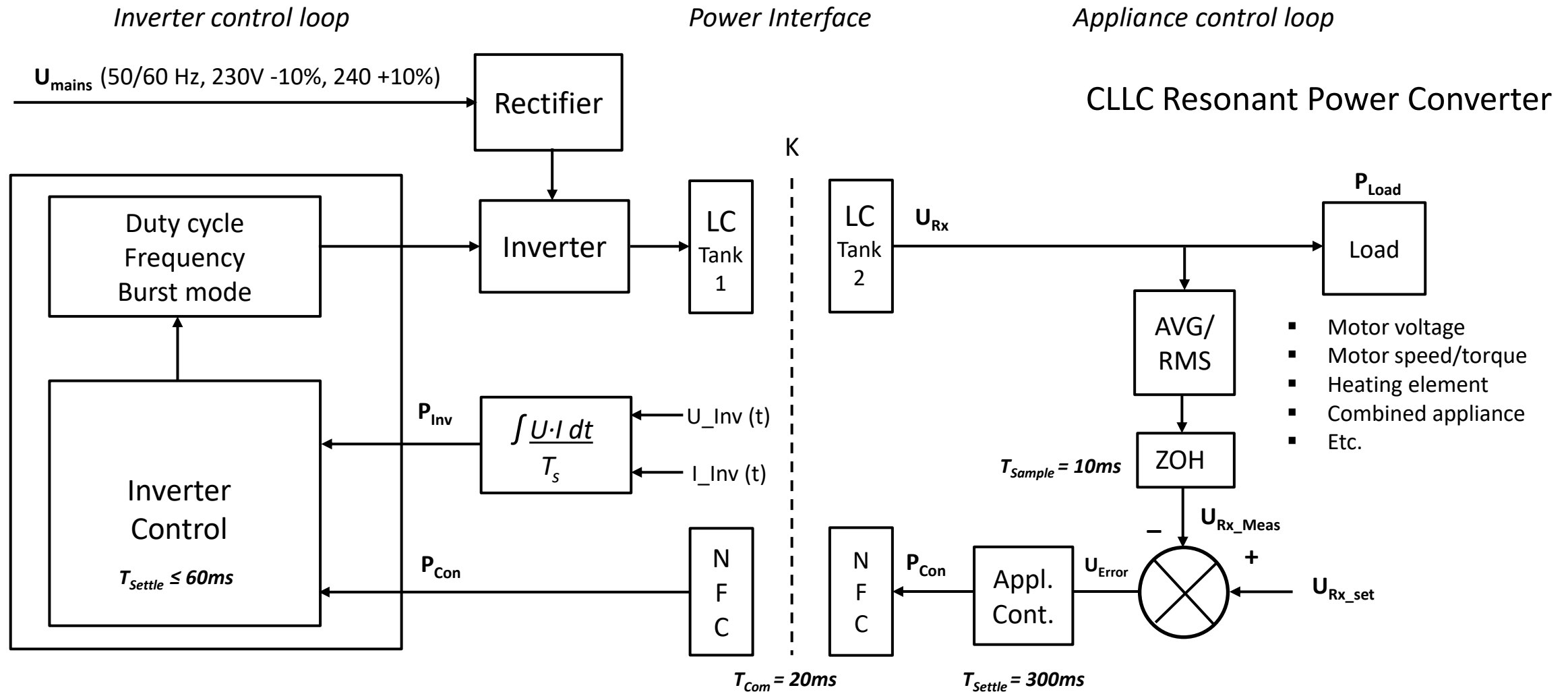Inner power control loop + outer appliance control loop



Power Control for Ki cordless kitchen system

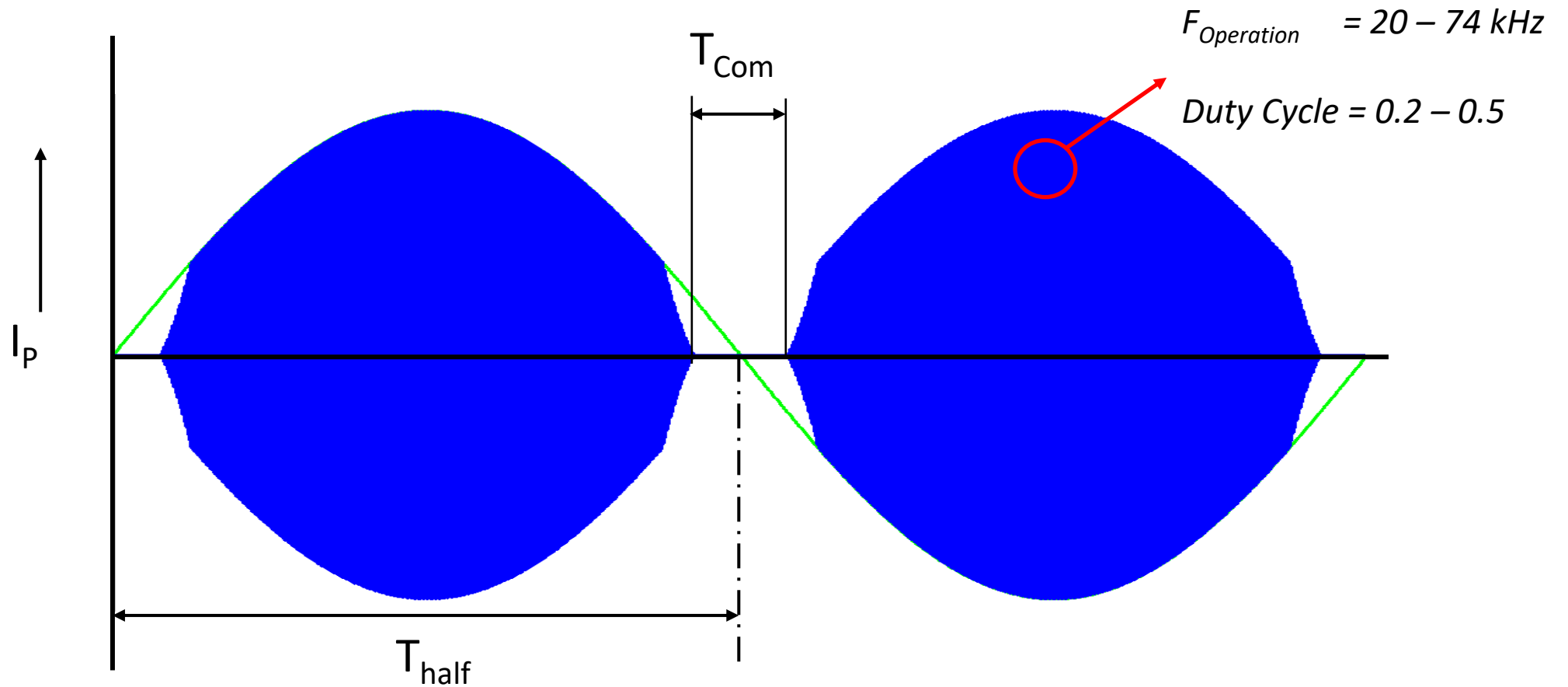
For $P_{out} > 50 \text{ W}$ -> Duty Cycle & Frequency control





Power Control for Ki cordless kitchen system

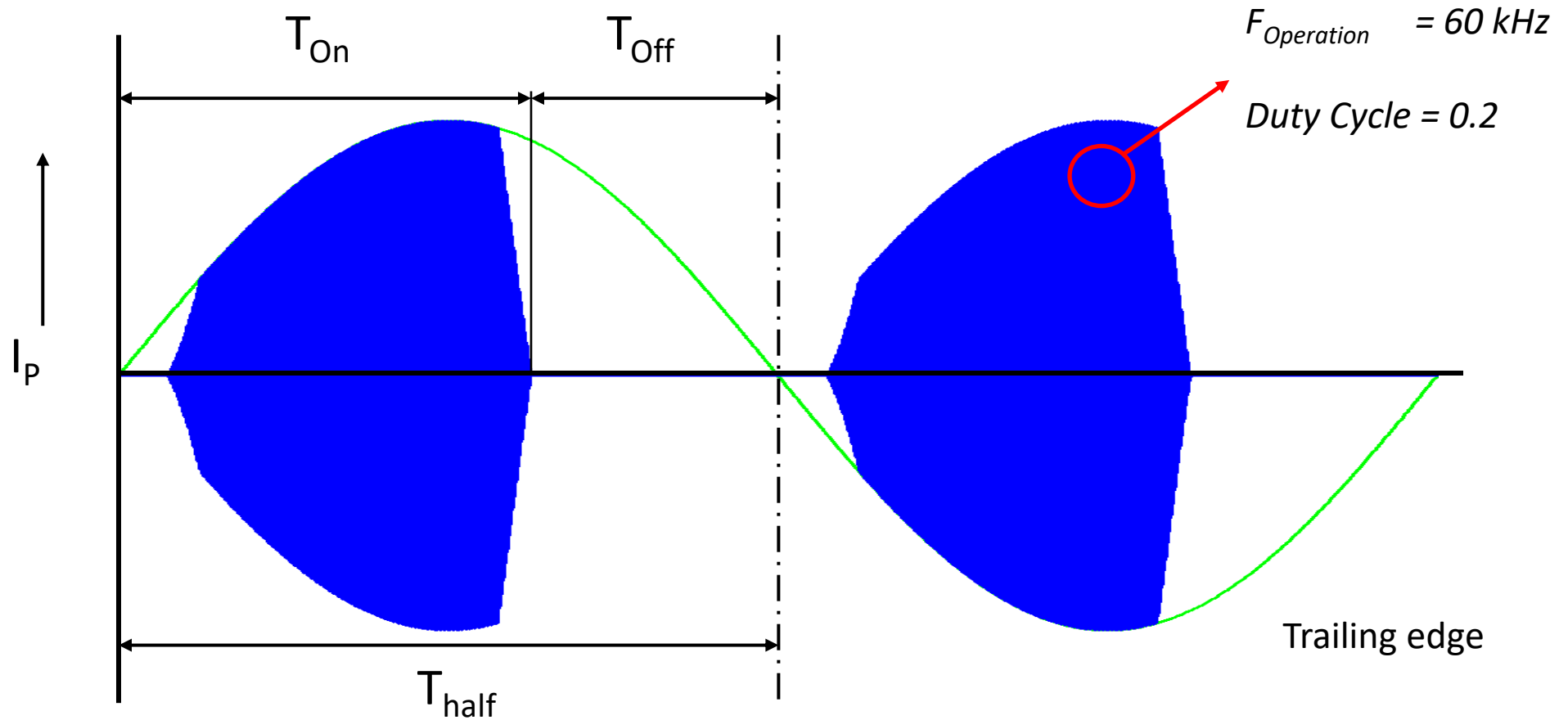
For $P_{out} < 50\text{ W}$ -> Burst Control @ fixed Frequency & Duty Cycle





AC analysis

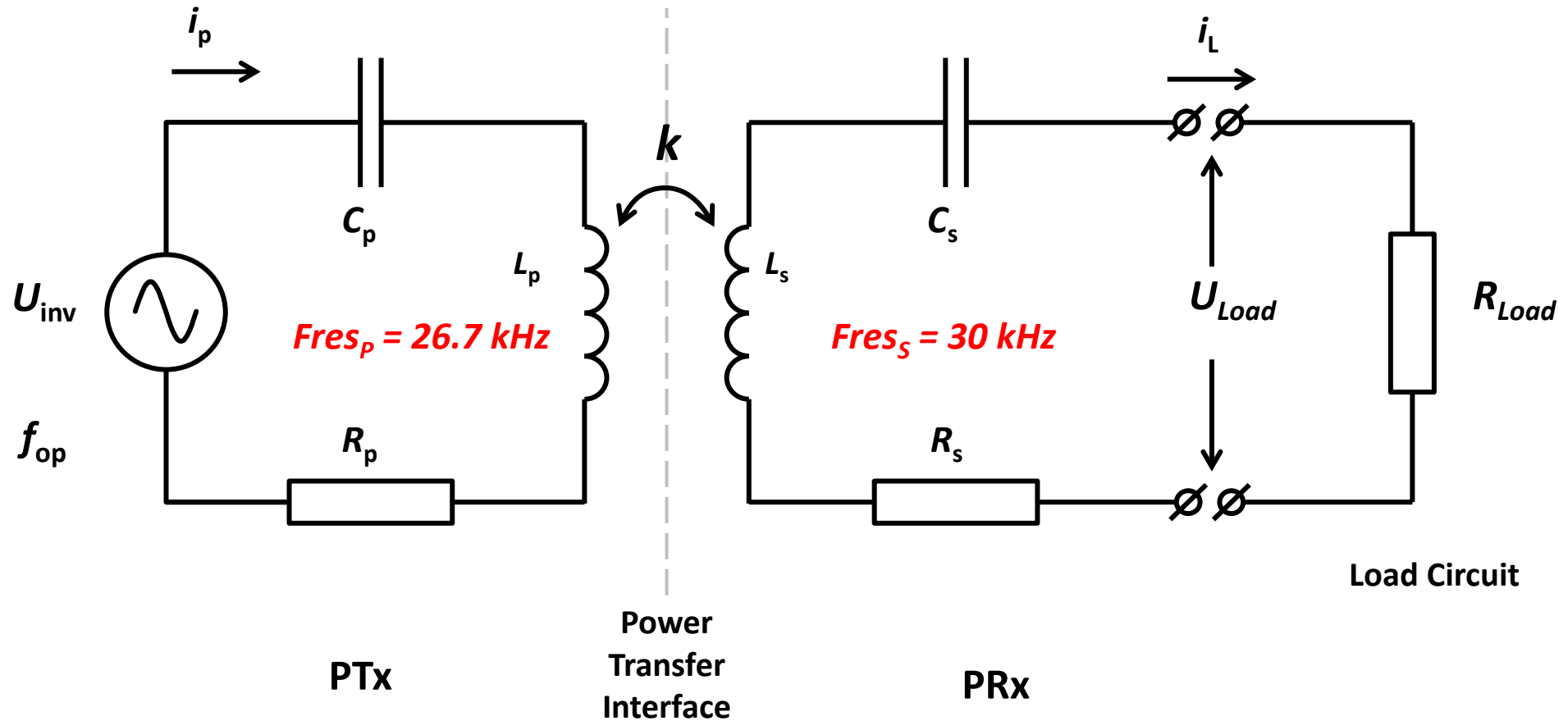
CLLC – network: Series CL in – Series LC out





AC analysis

First harmonic approximation (FHA)

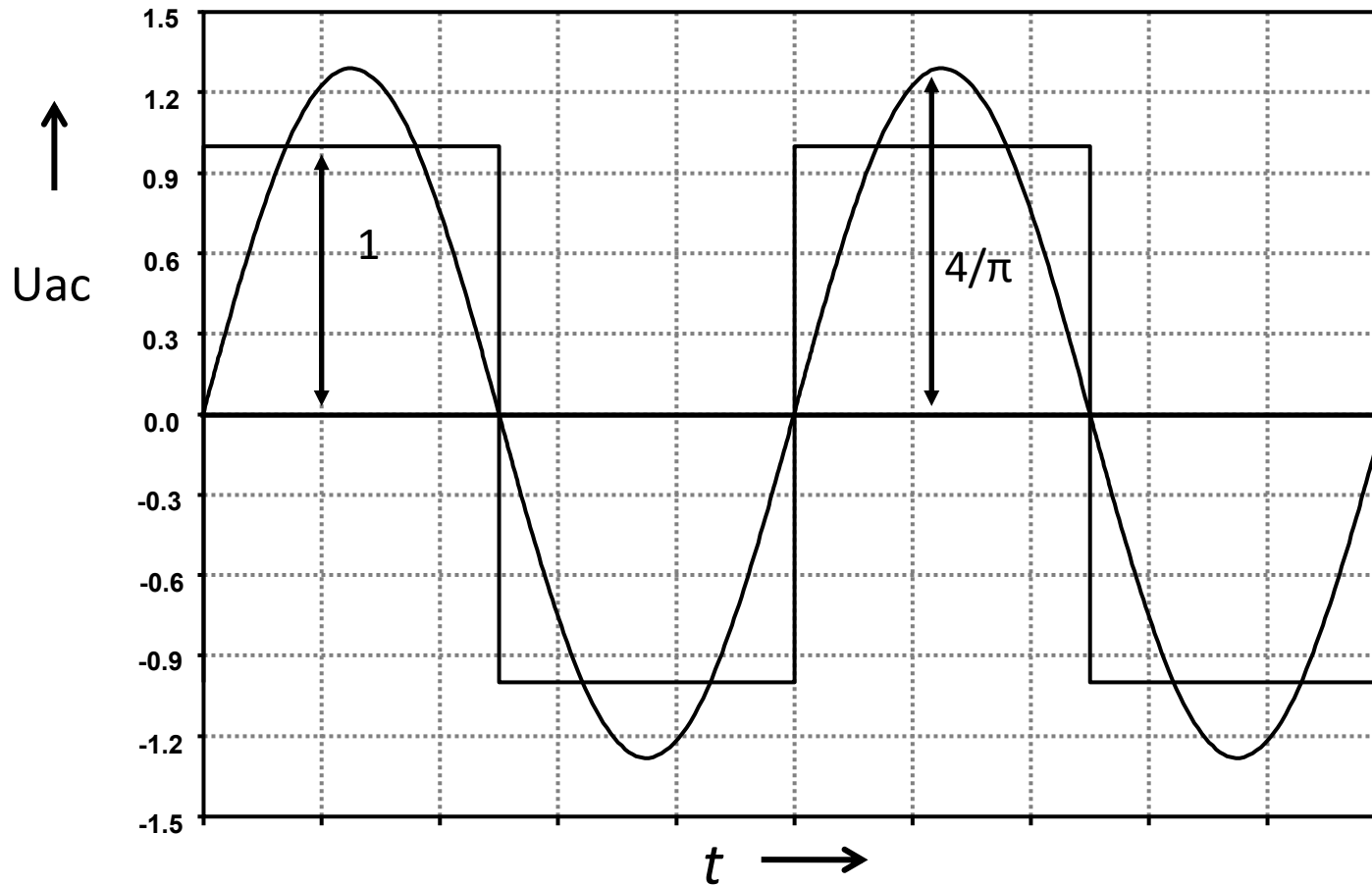

First Harmonic Approximation (FHA) is a modelling technique used to analyze & design resonant power converters.


The assumption is that only the **first harmonic** of the square wave contributes to the power transfer

$$U_{ac_n}(t) = \frac{4}{n \cdot \pi} \sin n \omega t$$


AC analysis



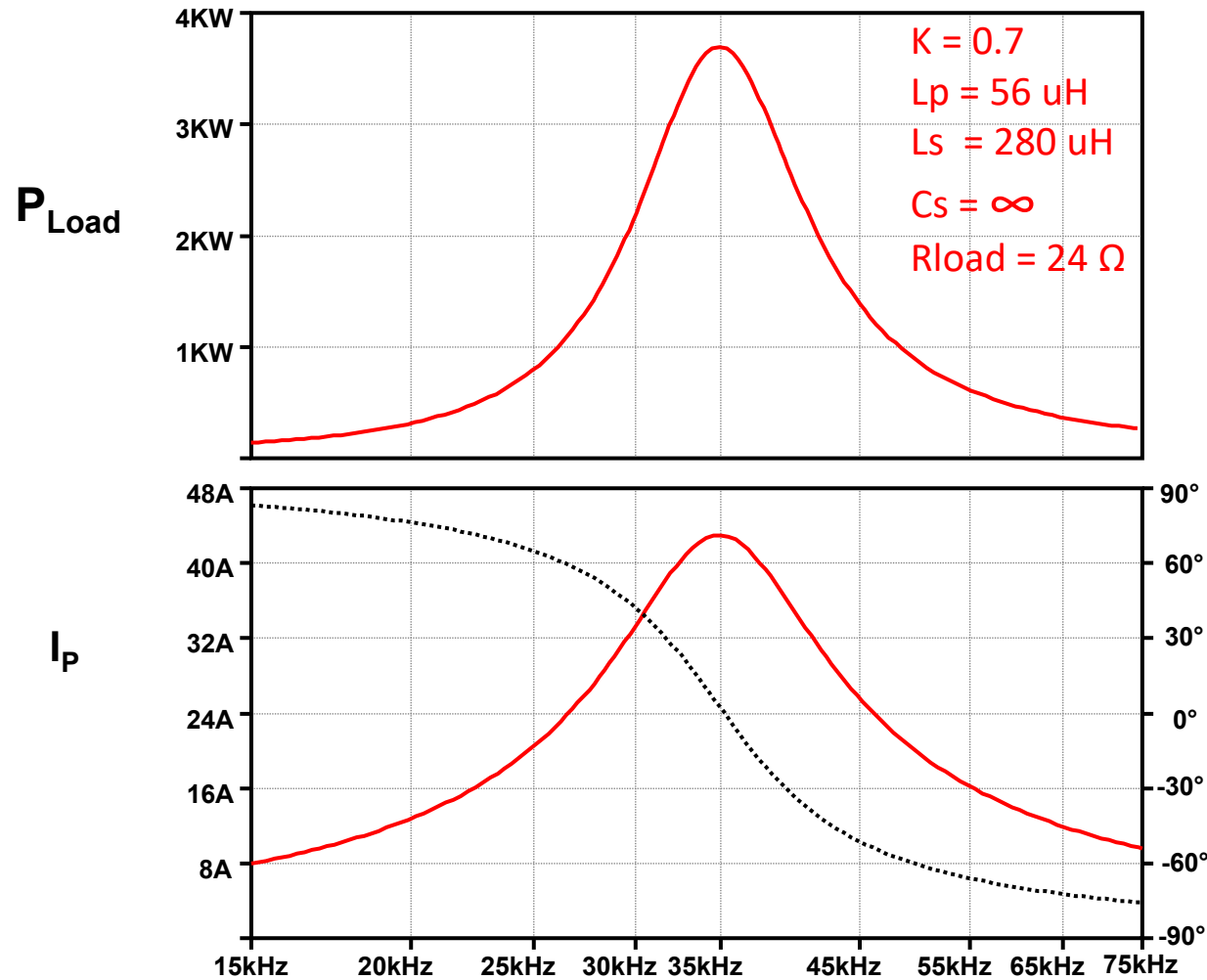Bode plots General Induction hob vs. Ki cooktop case (CLL vs. CLLC)



General Induction Hob (CLL)

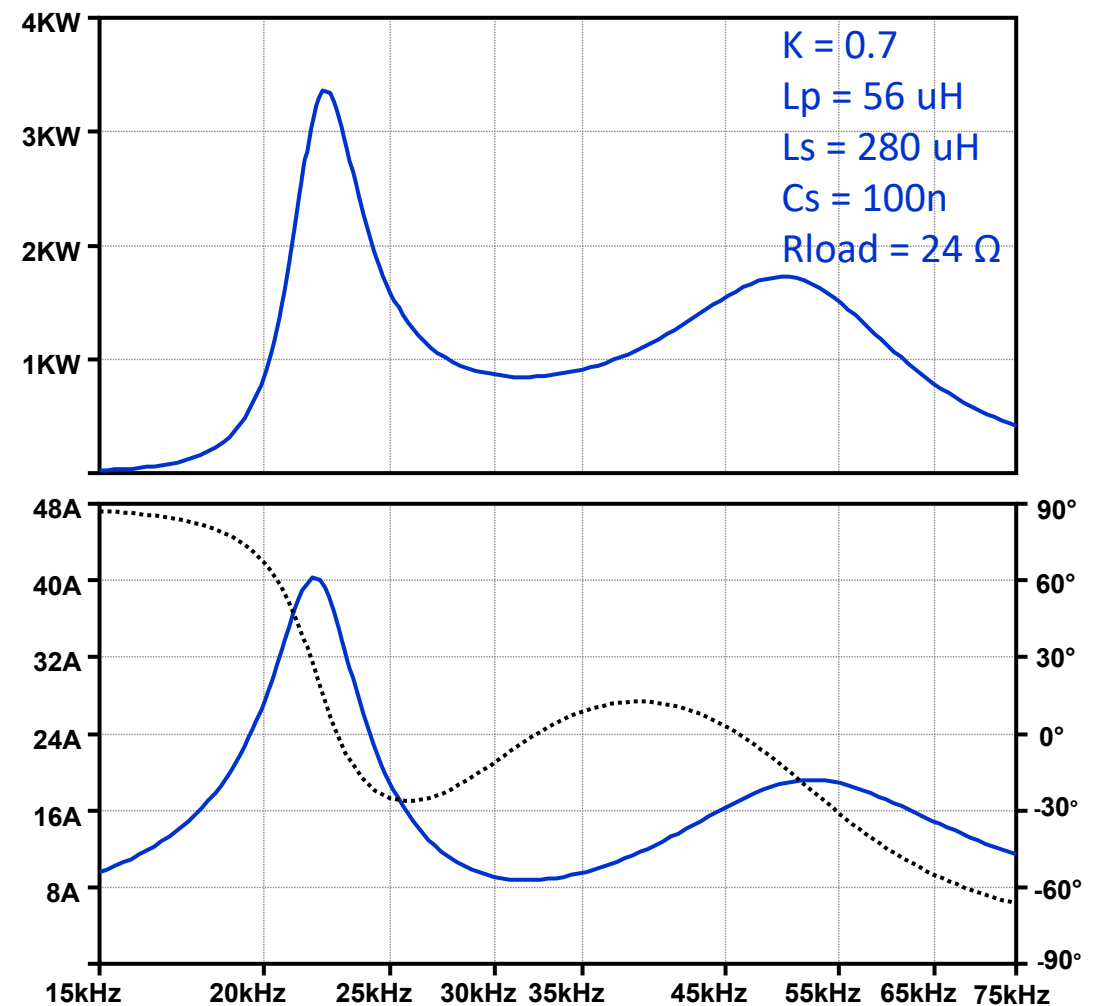


Ki cooktop system (CLLC)


AC analysis



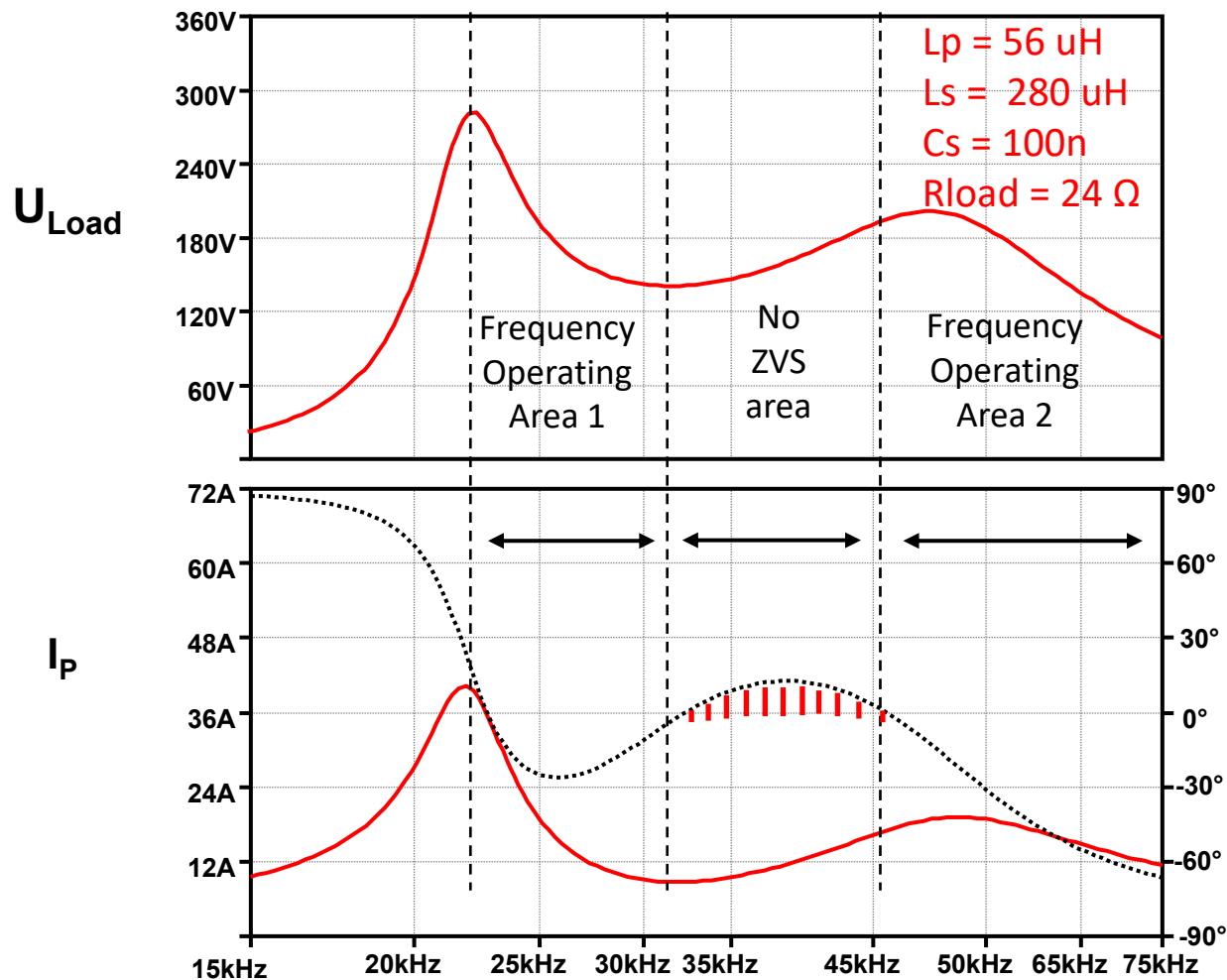Bode plots Ki cooktop case vs. concealed case ($K = 0.7$ vs. $K = 0.34$)




Ki cooktop case ($K=0.7$)

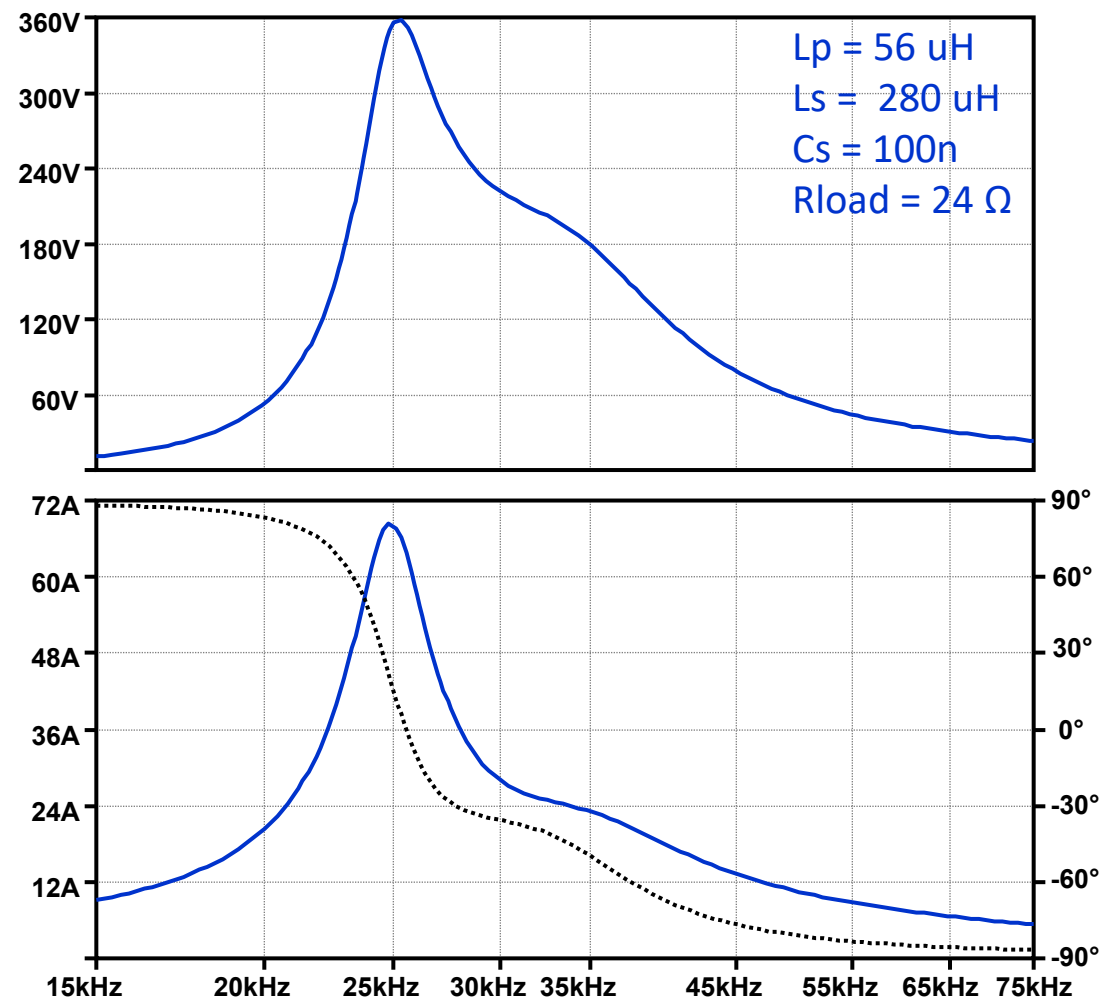

Ki concealed case ($K= 0.34$)

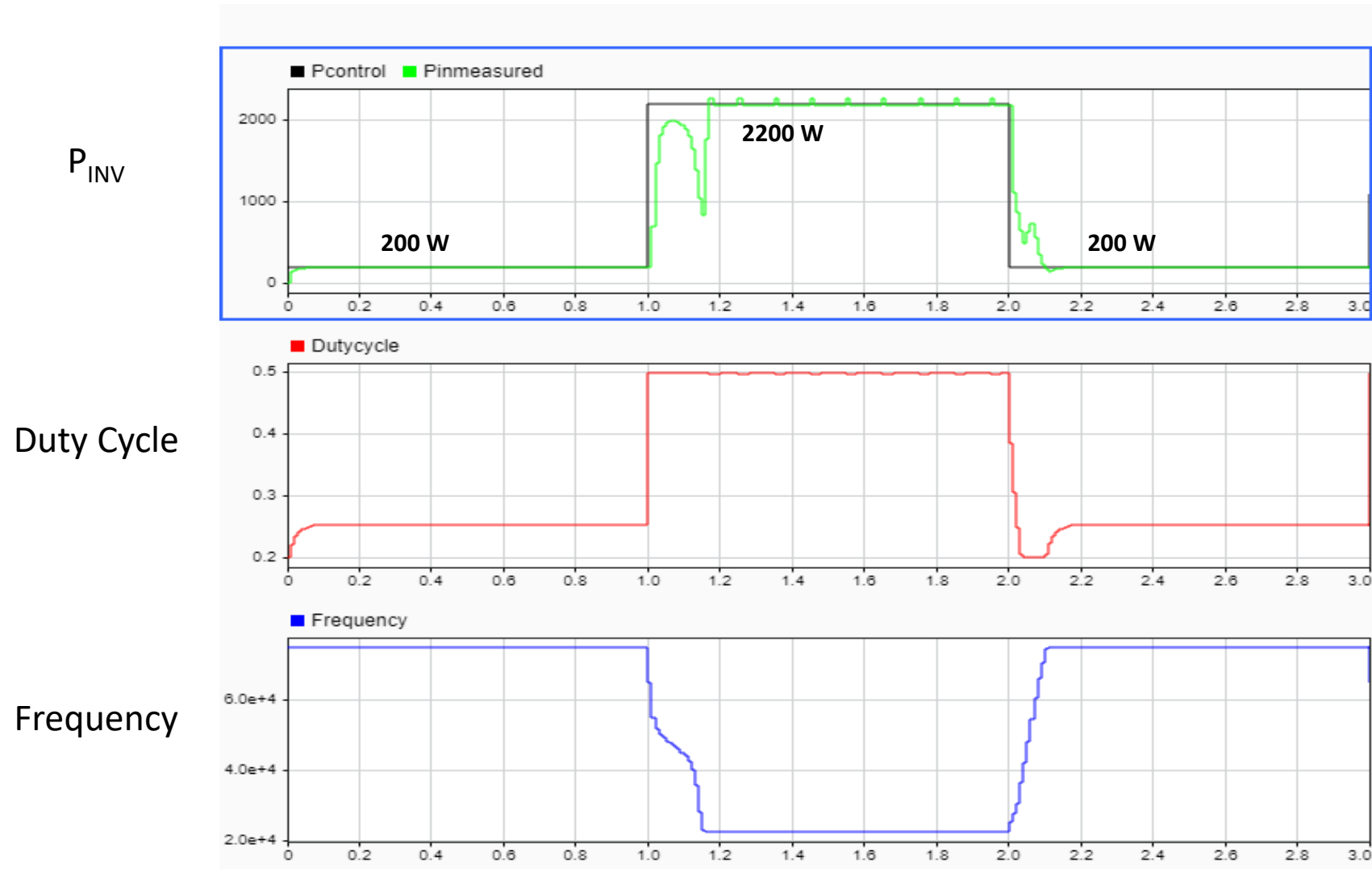Power step response Ki cooktop case for K= 0.7



Conclusion



- In this presentation the proposition and basic operation principle of the Ki cordless kitchen system was discussed
- However, this presentation did not cover:
 - NFC system:
 - Communication protocol
 - Power harvesting
 - Control dynamics
 - Foreign Object Detection (FOD)
 - Global Safety, Radio & EMC regulations
 - Ki Test tools & Compliance program
 - Licensing programs
 - Reference designs
 -






Supporting slides

Ki Development tools




Development Receiver

Reference Receiver
(RRD1 - RRD8)

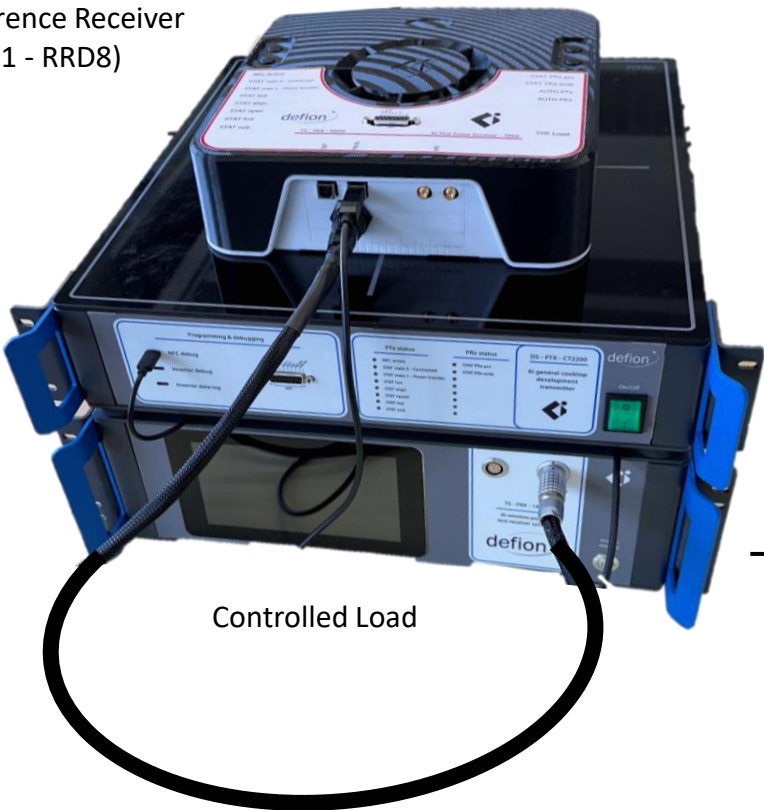

PTx DUT (device under test)

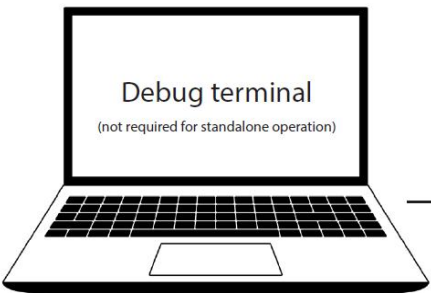

Development Transmitter

PRx DUT (device under test)



Wireless power and NFC comm



Development PTx

resillon & defion
Assure. Secure. Innovate.

PTx coil parameters for half bridge inverters




Transmitter	Guaranteed Power [kW]	Z Coil-2-coil [mm]	fp nom [kHz]	Tx coil diameter [cm]	Lp [μH]
Cooktop case	2.20	12	26.8	18	56
Concealed case	2.20	32	30.0	21	60

Ki Reference Receiver Designs (RRD's)



Fres = 30 kHz

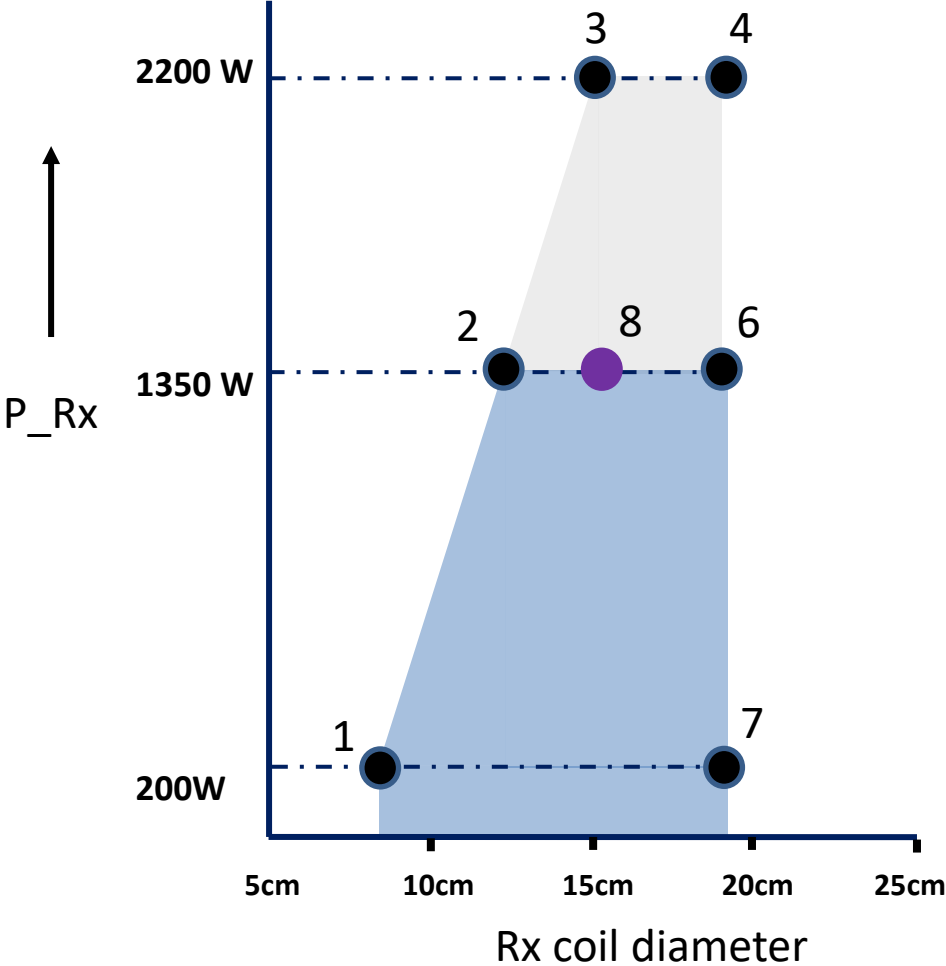

RRD #	P_Rx (W)	Ø (cm)	Ls (uH)	Uload (V)	Rload (Ohm)
1	200	8	390	115	66
2	1350	12	450	230	39
3	2200	15	280	230	24
4	2200	18	220	230	24
5					
6	1350	18	220	230	39
7	200	18	220	115	66
8	1350	15	280	230	39




- Complexity vs. Flexibility
- Both near zero power transfer and high-power transfer possible

- Price!
- Not in scope for “230V” region's

Ki Power chain in more detail

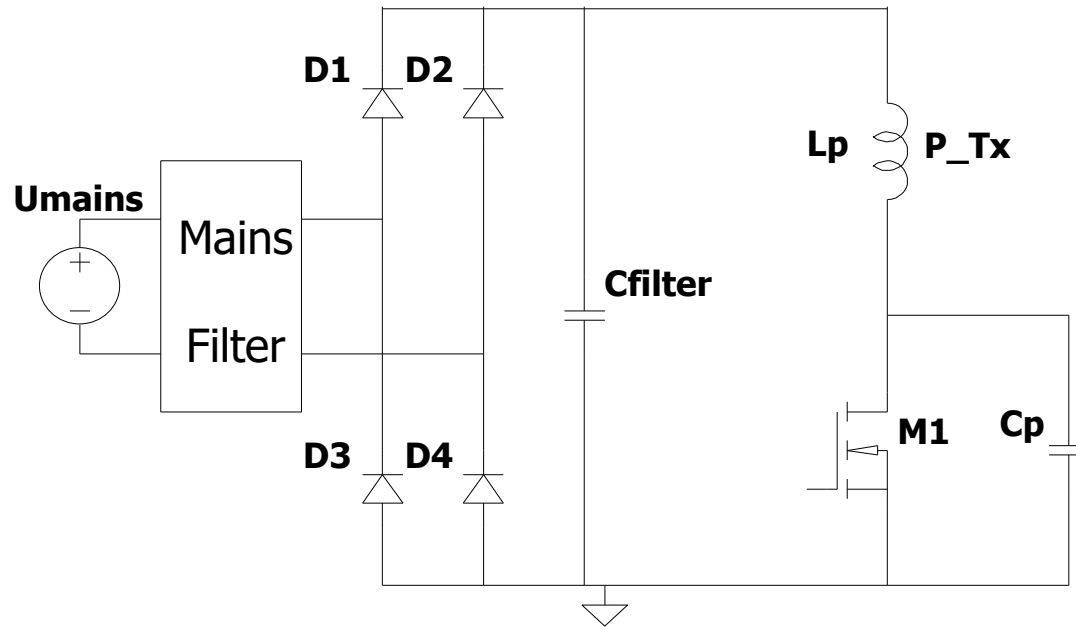Transmitter implementation – Single switch



“Parallel” resonant

Topology of choice for the managers ☹️

- Price vs. Complexity


But

- Optimized to provide high power, but in a small control window
- Near zero power transfer still a challenge, not proven yet



Power Control for Ki cordless kitchen system

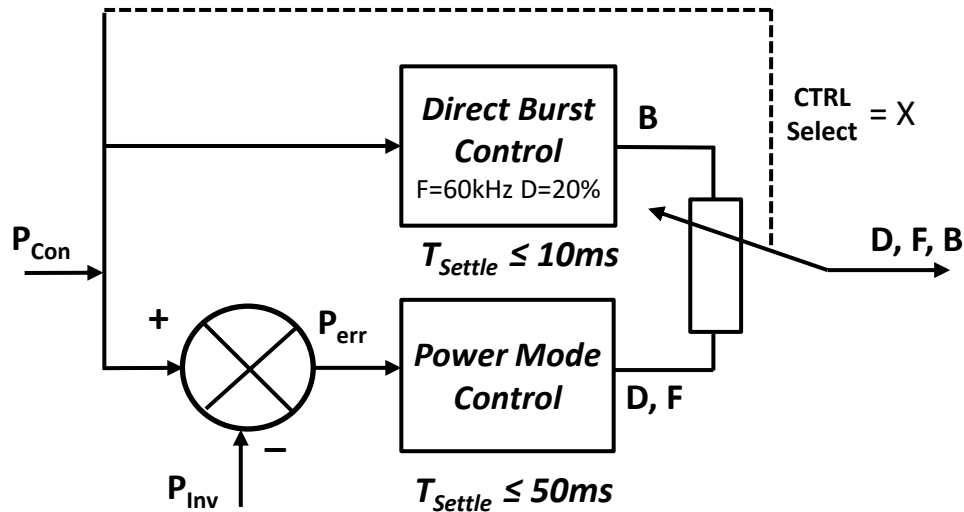
For $P_{out} < 50\text{ W}$ -> Burst & Duty Cycle Control @ fixed frequency



$$B_{pwm} = B_{\text{Direct_Burst_Control}} * X + B_{\text{Power_Mode_Control}} * (1-X)$$

$$D_{pwm} = 20\% * X + D_{\text{Power_Mode_Control}} * (1-X)$$

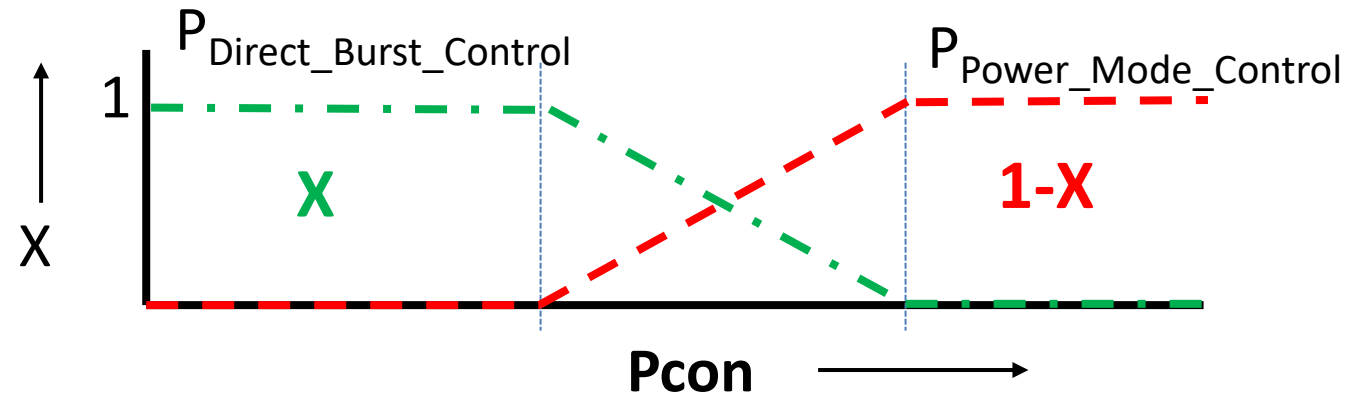
$$F_{pwm} = 60\text{kHz} * X + F_{\text{Power_Mode_Control}} * (1-X)$$





AC analysis

CLL – network: Series LC in – L out

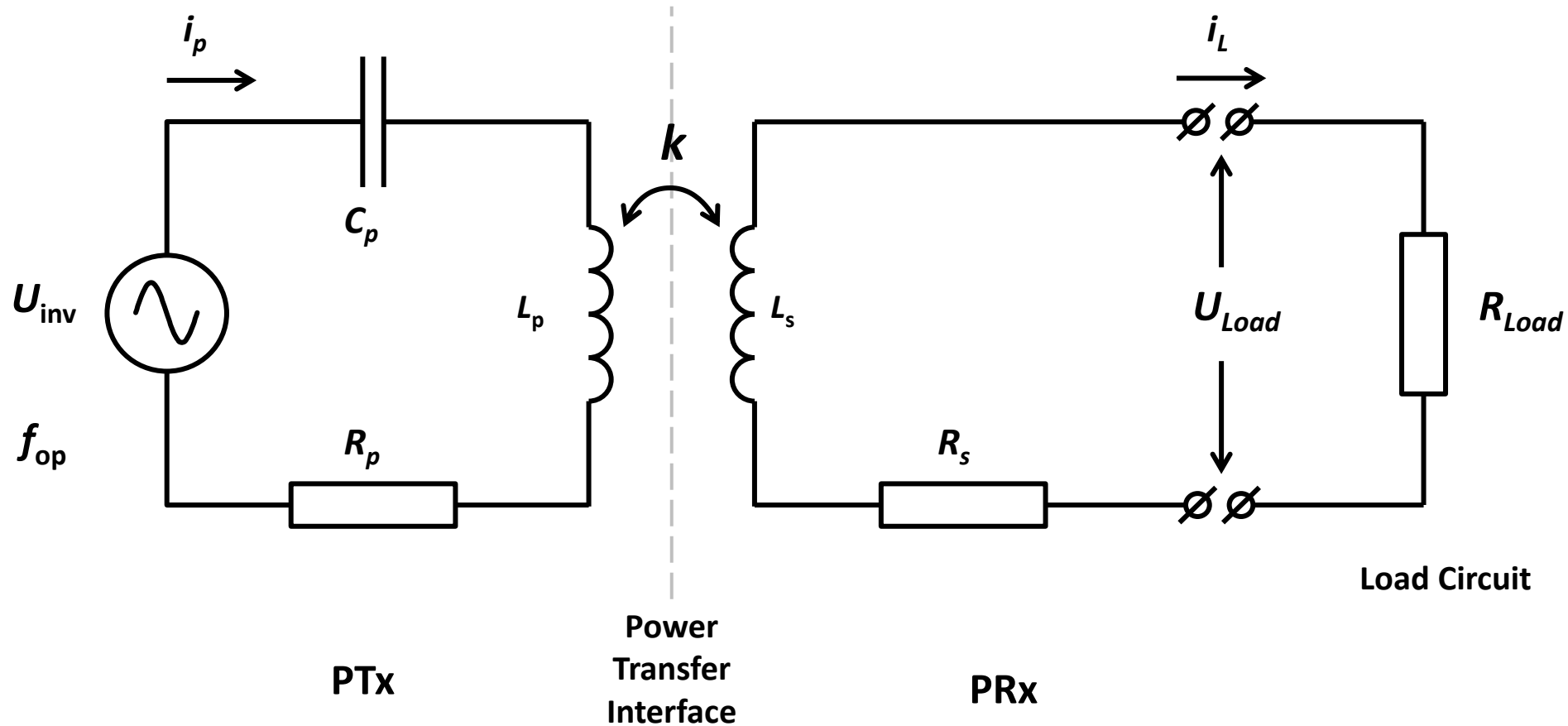



AC analysis

CLL versus CLLC – network: Efficiency

