



Power to the LED





Alex Snijder

Field Application Engineer

Wurth Elektronik Nederland

<u>Alex.snijder@we-</u> <u>online.com</u>

LED LIGHTING & TECHNOLOGY CONFERENCE 2019

DONDERDAG 28 NOVEMBER 2019

VAN DER VALK, EINDHOVEN

Agenda



- LED driver basics
- Schematic review
- EMI considerations
- Summery





The Würth Elektronik Group

Sales: 848 million € Employees: 8.300 * 2018





Printed Circuit Boards

Intelligent Power and **Control Systems**

Passive Components



Power Modules & Optoelectronics



Electromechanical Components



Automotive & eMobility



Wireless Connectivity & Sensors




LED LIGHTING & TECHNOLOGY CONFERENCE 2019 28 NOV · EINDHOVEN

Introduction to LED Drivers

How to switch a LED on



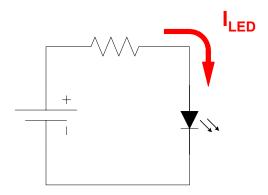

Well yes, it works!!! But....




Introduction to LED Drivers

Basic operation



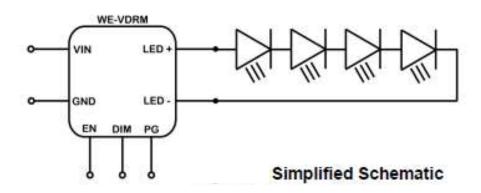- LED must be driven with current
- Switching regulators (buck,boost,buckboost) offer a more efficient solution
- LED can be connected in series, parallel, series-parallel, etc.
- Brightness adjustment through Analog/PWM/PFM dimming
- LED fault management



Magl³C LED Driver

General description

Features:

- LED Current capability: up to 450 mA
- Wide input voltage range: 4.5 V 60 V
- Drives 1 to 16 LEDs in series up to 60 V input
- Typical LED Current Accuracy ±3.5 %
- PWM Dimming
- Analog Dimming
- High contrast ratio (min. PWM current < 16 μs)
- · Integrated magnetics solution for ease of use
- Connectable in parallel for higher current operations
- Input under voltage lockout protection (UVLO)
- Temperature range: -40 °C to 125 °C

Package:

- TO-263-7
- RoHS & REACH compliant
- UL94V-0 mold material






Applications:

- Indoor lighting
- Outdoor lighting
- Industrial lighting

Application Diagram:

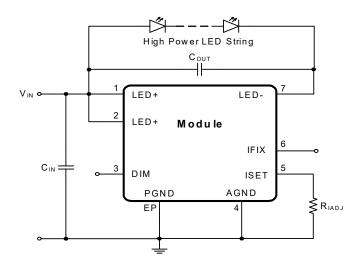




Introduction to LED Drivers

Basic operation






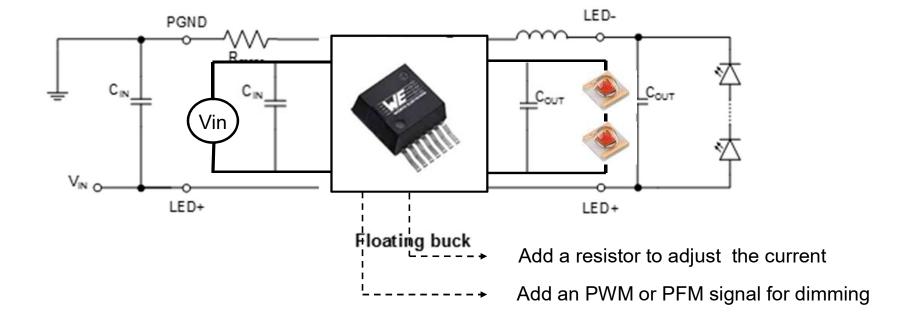

Magl³C LED Driver

Floating Buck Architecture

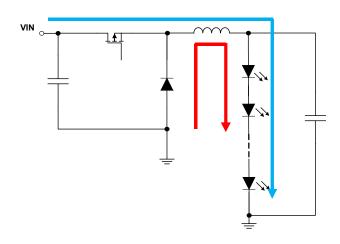


Traditional Buck

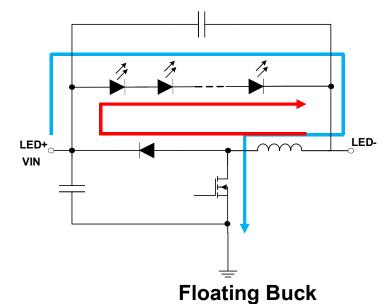- High side nMOS (=>complexity) or pMOS (=>size)
- LED always connected to GND








- Low side nMOSFET (easier and smaller design)
- Floating LED connection
- Regulation only during CCM
- Possible extension to other topologies

LED Drivers features

Dimming control



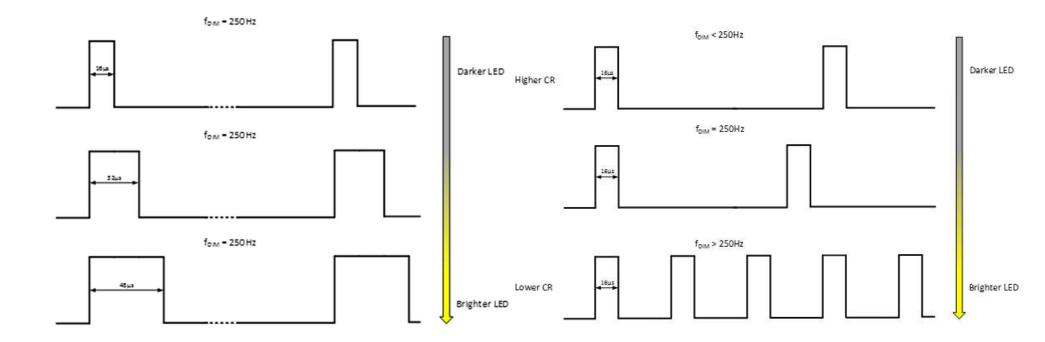


LED Drivers features

Dimming control





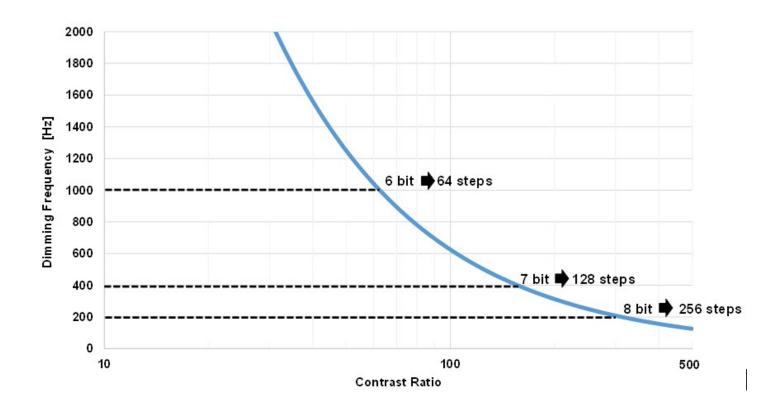

DD.MM.YYYY | Technical Academy | Public | <TITLE>

© All rights reserved by Wurth Electronics, also in the event of industrial property rights. All rights of disposal such as copying and redistribution rights with us.

9

Build your own LED driver

Reference Design: Multi Color LED Driver






Description

- 4 Channel LED Driver (can be extended by connecting daughter board)
- 1-26 LEDs with 1,8V each in series per channel (depending on LED forward voltage)
- Upto 450mA per channel driving current
- PWM dimming method controlled by PIC16F1527 microcontroller
- Intensity of each channel can be adjusted individually (dimming 0-100%)
- Color mixing with four channels and RGBW LEDs
- Dimming by potentiometer, button or Bluetooth control (2608011024000)
- Dimming profiles and colors can be stored
- LED Driver: Magl³C Power Module 172 946 001
- Conducted and radiated EMI compliant (EN55015)
- Good thermal behavior



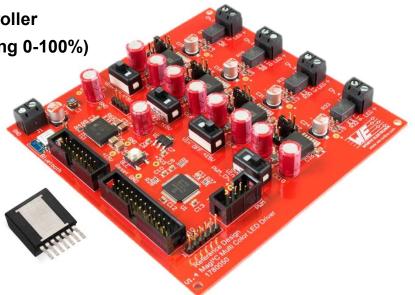


Reference Design: Multi Color LED Driver

Block Diagram





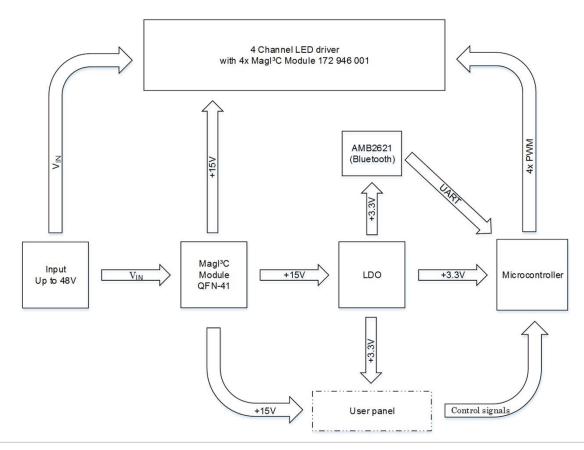


DD.MM.YYYY | Technical Academy | Public | <TITLE>

11

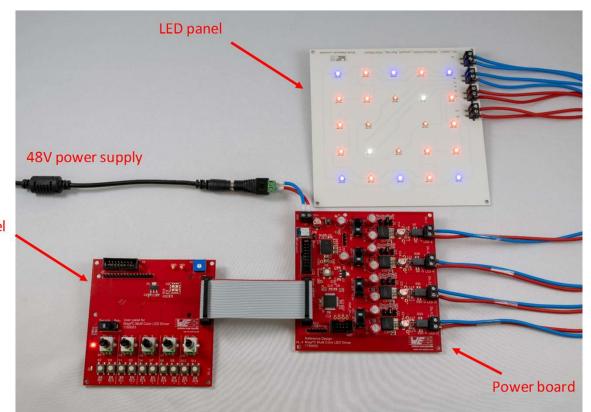Reference Design: Multi Color LED Driver Power Board, User Panel and LED Panel








User panel

DD.MM.YYYY | Technical Academy | Public | <TITLE>

@ All rights reserved by Wurth Electronics, also in the event of industrial property rights. All rights of disposal such as copying and redistribution rights with us.

LED driver reference design



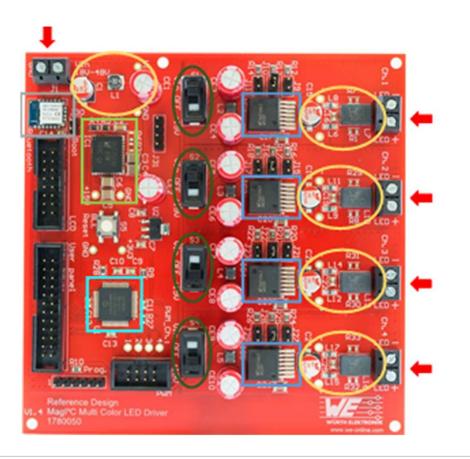


- 18-48V_{In}; 1,8-V_{in} V_{out}; up to 450mA
- LDHM LED Step Down High Current Module 172946001
- VDRM Variable Step Down Regulator Module QFN-41 171021501
- PIC16F1527 Microcontroller
- Bluetooth 4.2 Smart Module (260811024000)
- Switch between V_{In}, Off and +15V
- Input and Output Filter
- Robust screw terminal for V_{In} and V_{Out}

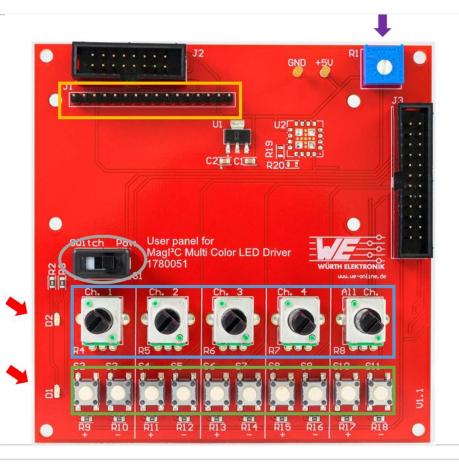Reference Design: Multi Color LED Driver User Panel








- Potentiometer for LCD contrast
- Possibility for an LCD to show dimmingratio per channel
- Switch between potentiometer or button operation
- LED for indicating potentiometer or button operation
- · Potentiometer for LED dimming
- Buttons for LED dimming

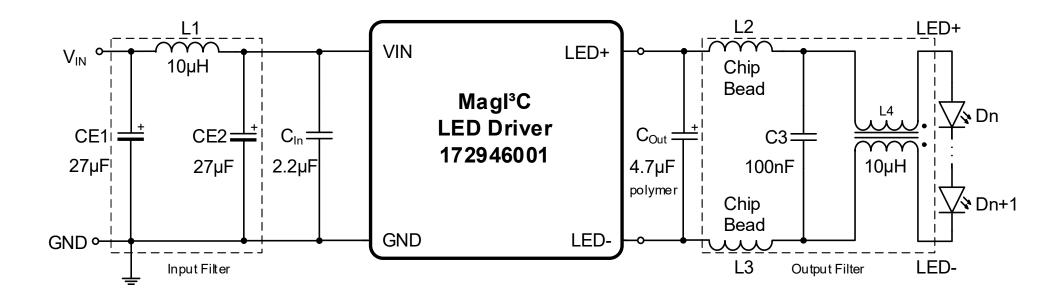Multi Color LED Driver Single LED Channel EMI Filter








Multi Color LED Driver

Single LED Channel EMI Filter





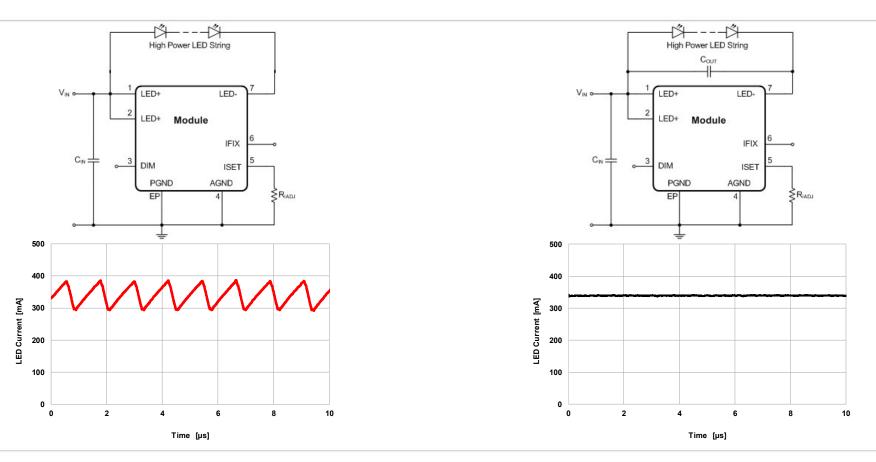


Multi Color LED Driver

Single LED Channel schematic





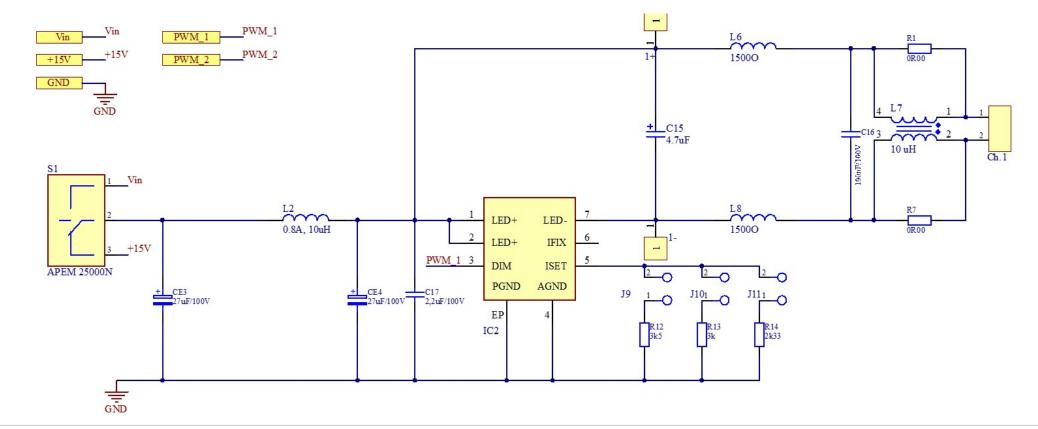

DD.MM.YYYY | Technical Academy | Public | <TITLE>


www.we-online.com

Multi Color LED Driver

Single LED Channel EMI Filter






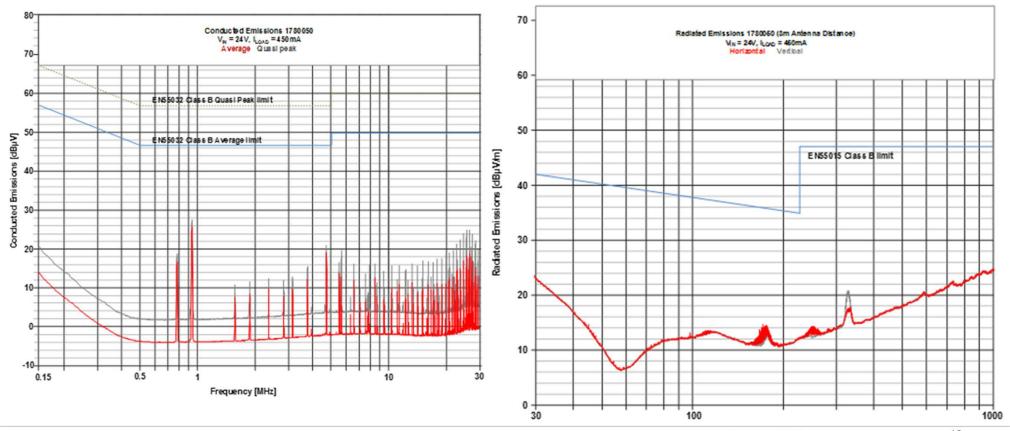

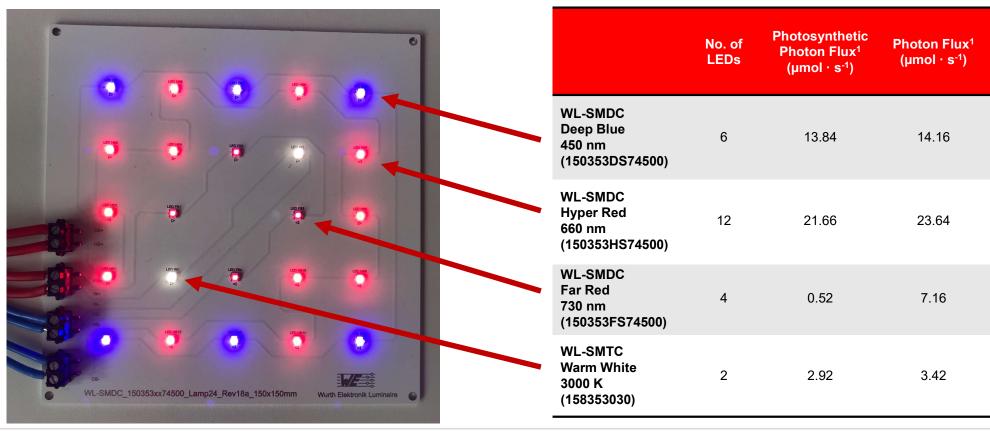Reference Design: Multi Color LED Driver LED Panel








LED Selection

REDEXPERT® - Horticulator





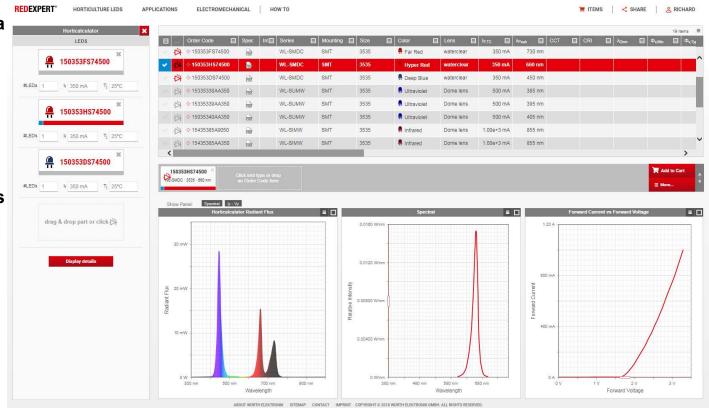- Design custom light spectra
- See electrical parameters
- See quantum output parameters
- Quick access to data sheets
- Order free samples



The data only serves as a reference and does not imply any warranty. The simulated figure is according to the test conditions above. The values and the representation may be changed and/or updated without notification. 6
This document is strictly confidential. It shall not be reproduced, modified, adapted, or forwarded without the written permission of Würth Elektronik eiSos GmbH & Co. KG.

Summery





- To drive LED an LED driver is preferred
 - Enables dimming control
 - Higher efficiency
- EMC challenges around an LED driver design
 - Differential mode noise LC or PI filters
 - Common mode noise Common mode chokes
- Typical applications
 - Horticulture
 - General lighting applications
 - Street signs





