

20 juni 2017  
1931 Congrescentrum Den Bosch

**POWER  
ELECTRONICS** 2017

Electromechanics and Power Electronics Group

## 3–5 Level Bidirectional Dual Active Bridge DC–DC Converter

Georgios Sfakianakis, MSc

June 20, 2017

H.Huisman, J.Everts, E.A.Lomonova



**ADEPT**


ADvanced Electric Powertrain Technology

**TU/e**


Technische Universiteit  
**Eindhoven**  
University of Technology

**Where innovation starts**

# Introduction

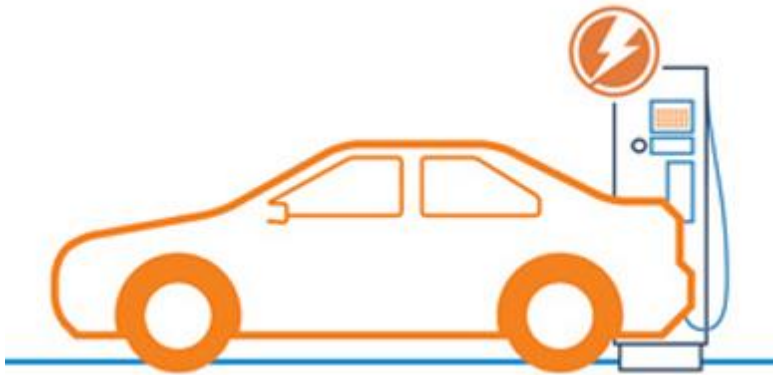

Source: "abb.com"

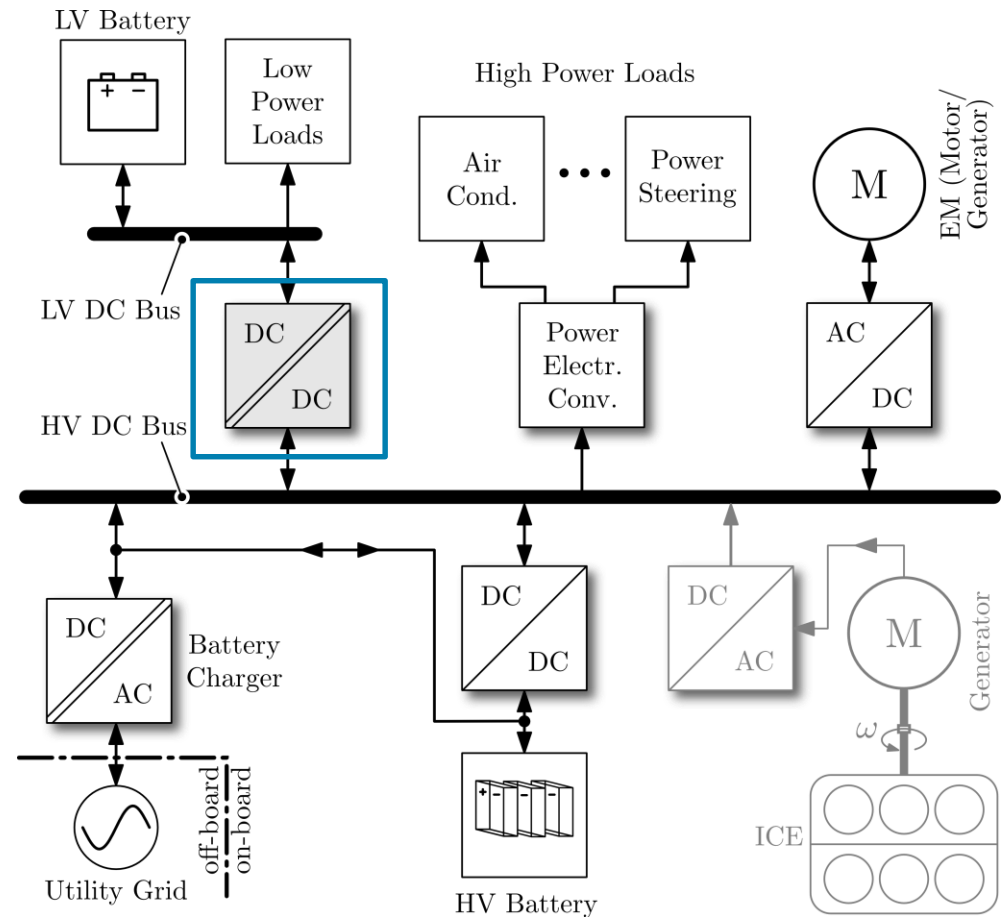

## ► Specifications


- 8-16 V<sub>DC</sub> (LV Side)
- 175-450 V<sub>DC</sub> (HV Side)
- 200 A (LV DC current)

## ► Motivation

- Single Stage implementation
- Multi Objective Optimization (MOO) of the converter
- Comparison with Dual Stage implementation


## ► Dual Active Bridge

- Soft-Switching
- Galvanic Isolation

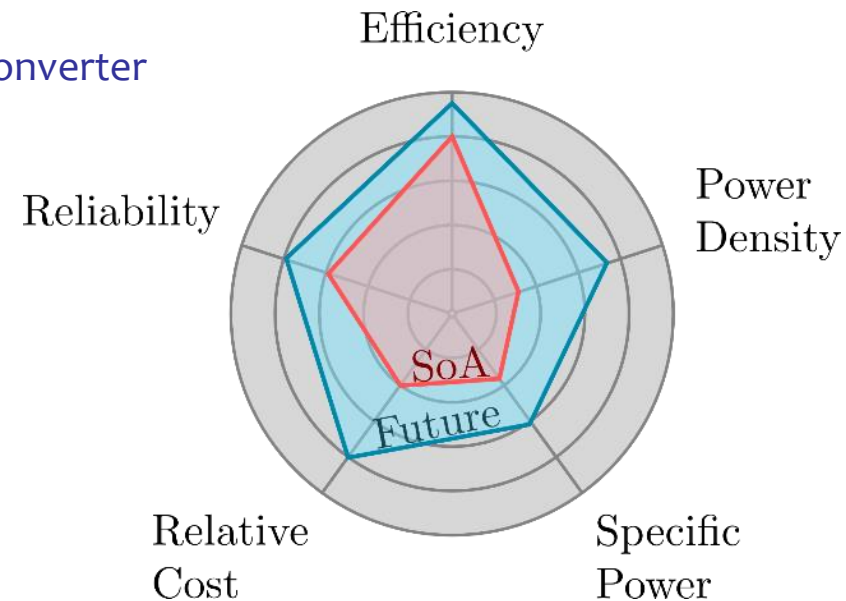


- ▶ The Dual Active Bridge (DAB)
  - Operating Principle
  - 3-5L DAB
- ▶ Switching Control Analysis
  - Zero voltage switching (ZVS)
  - Piecewise linear analysis
  - Switching modes and mode selection
- ▶ Modulation Strategy
- ▶ Experimental Results: Proof of concept
- ▶ Comparative Evaluation ( 3-3L vs 3-5L DAB)
- ▶ Conclusions

# The Dual Active Bridge

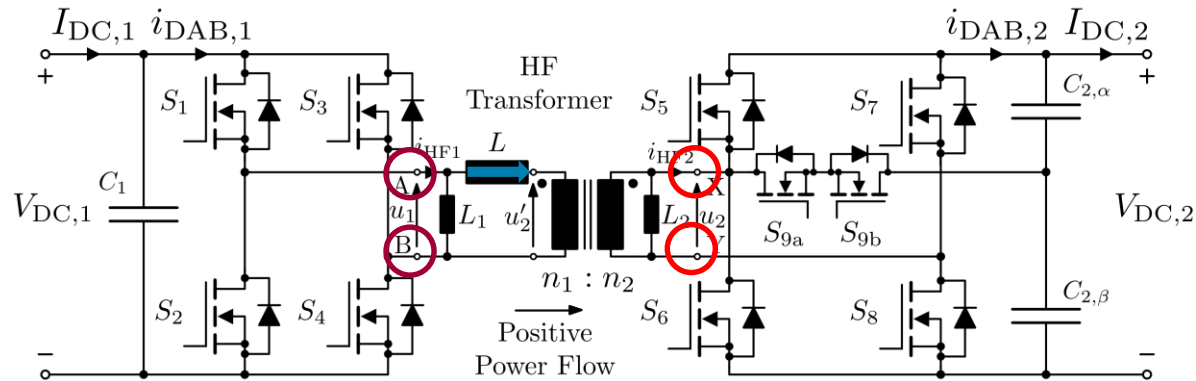

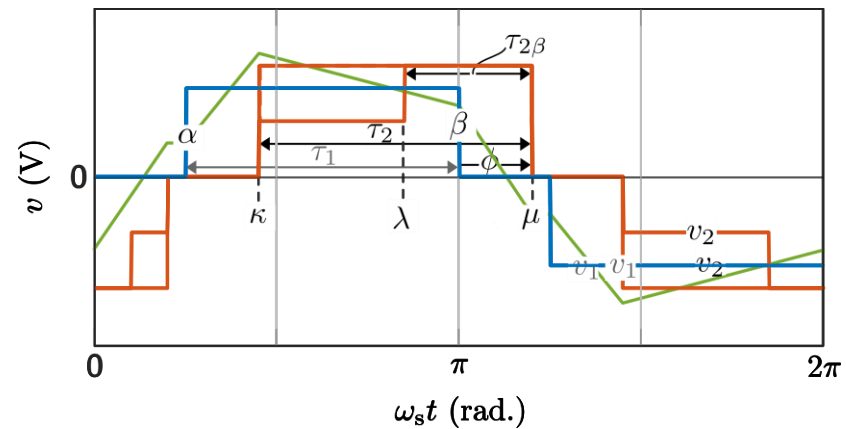
Control Variables  
 $\tau_1$ ,  $\tau_2$ ,  $\tau_{2B}$  and  $\phi$



# Zero Voltage Switching (ZVS)


*T2: ZVS turn-off*

*T1: ZVS turn-on*

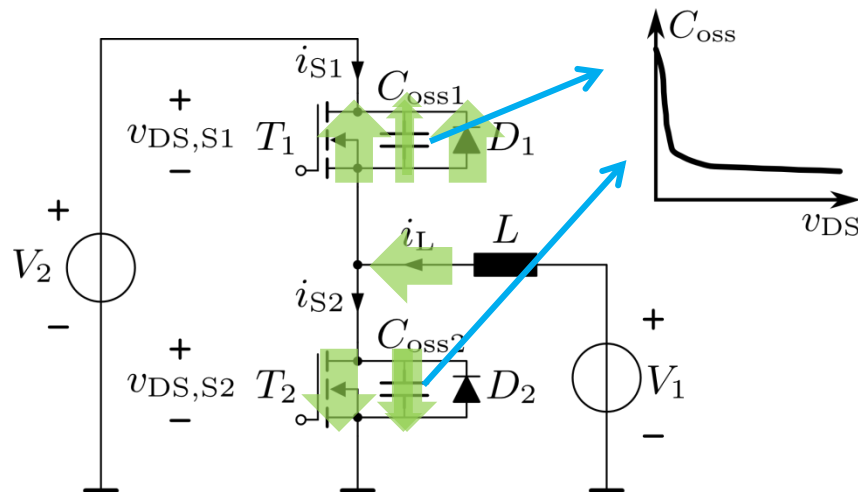

$$Q_{av,A} \geq Q_{oss,S}$$


$$Q_{av,B} \geq Q_{oss,S}$$

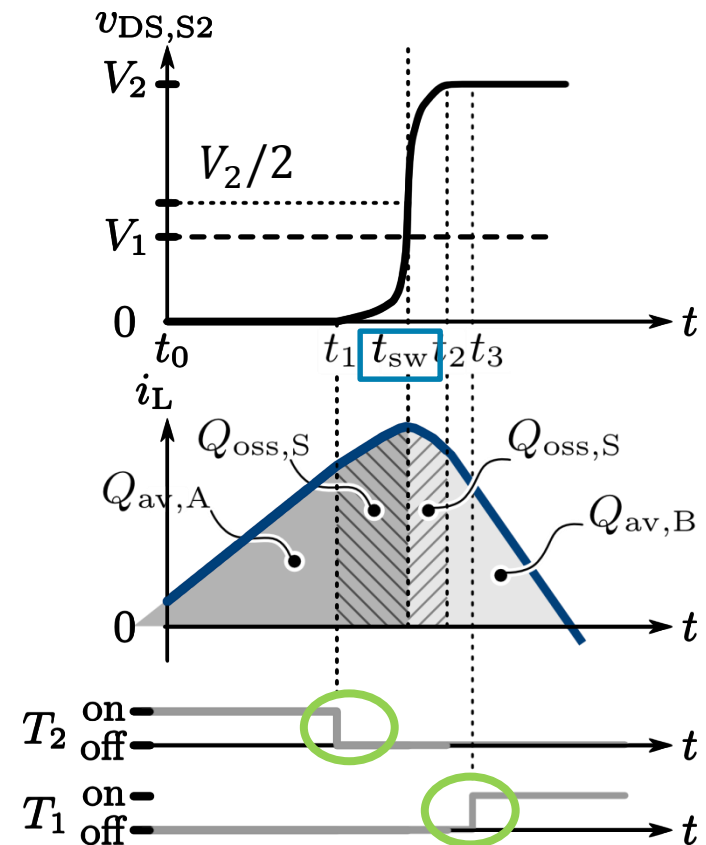

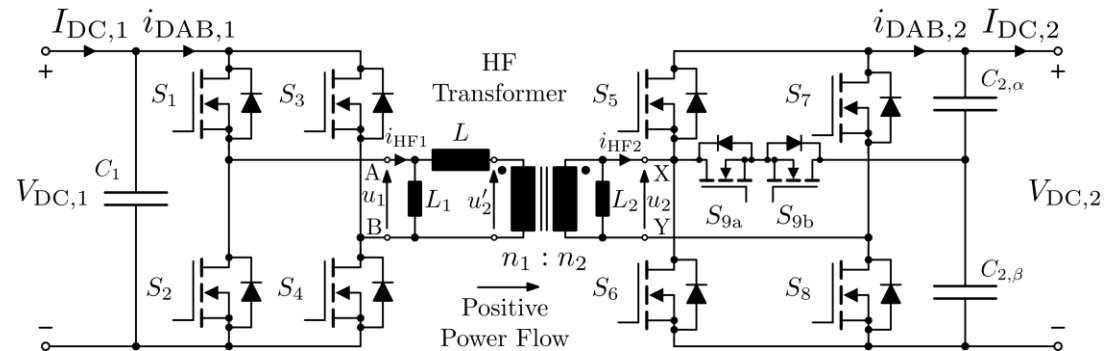
## ► Piecewise linear

$$\frac{di_L(t)}{dt} = \frac{v_1(t) - v'_2(t)}{L}$$

$$\frac{di_{L_1}(t)}{dt} = \frac{v_1(t)}{L_1} \quad \frac{di_{L'_2}(t)}{dt} = \frac{v'_2(t)}{L'_2}$$



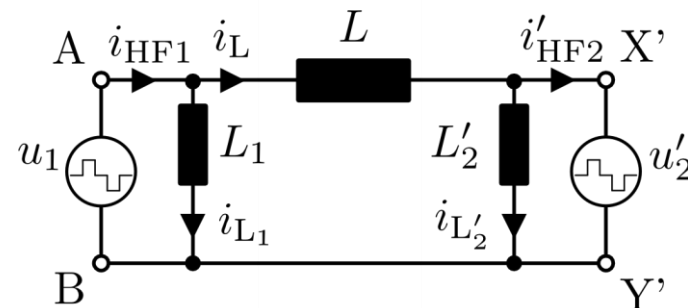
## ► 24 possible modes (i.e. different sequences of the voltage edges)




► Mode selection (non linear constrained minimization)

- Soft-switching constraints
- Input current
- Objective function:
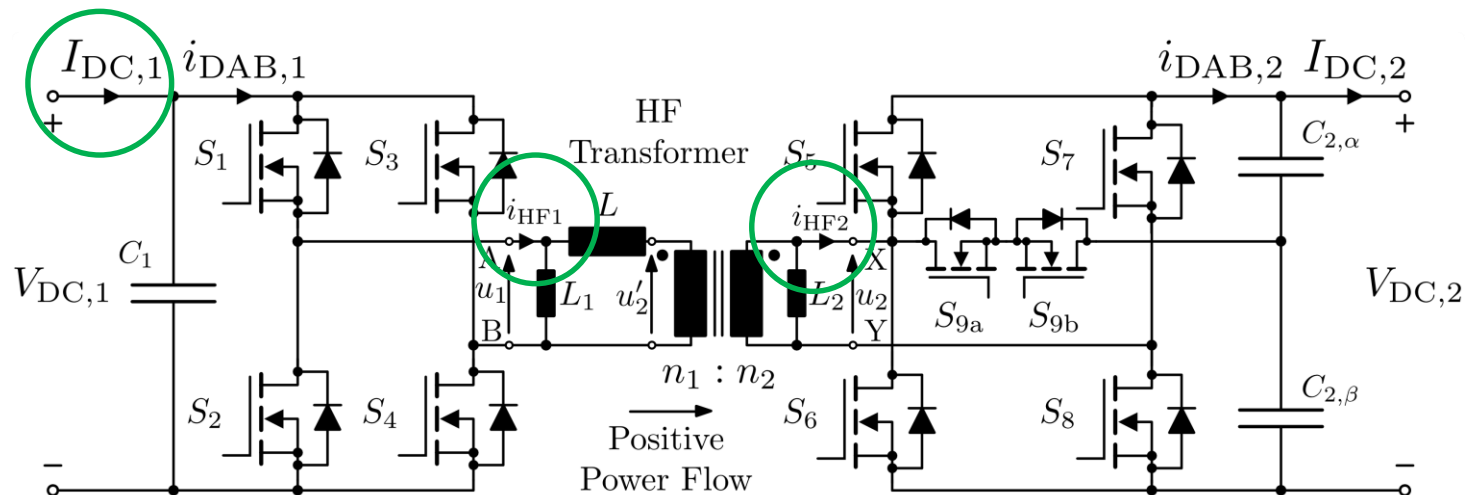
$$f_{\text{obj}} = I_{\text{RMS,HF1}}^2 + \frac{I_{\text{RMS,HF2}}^2}{N^2}$$






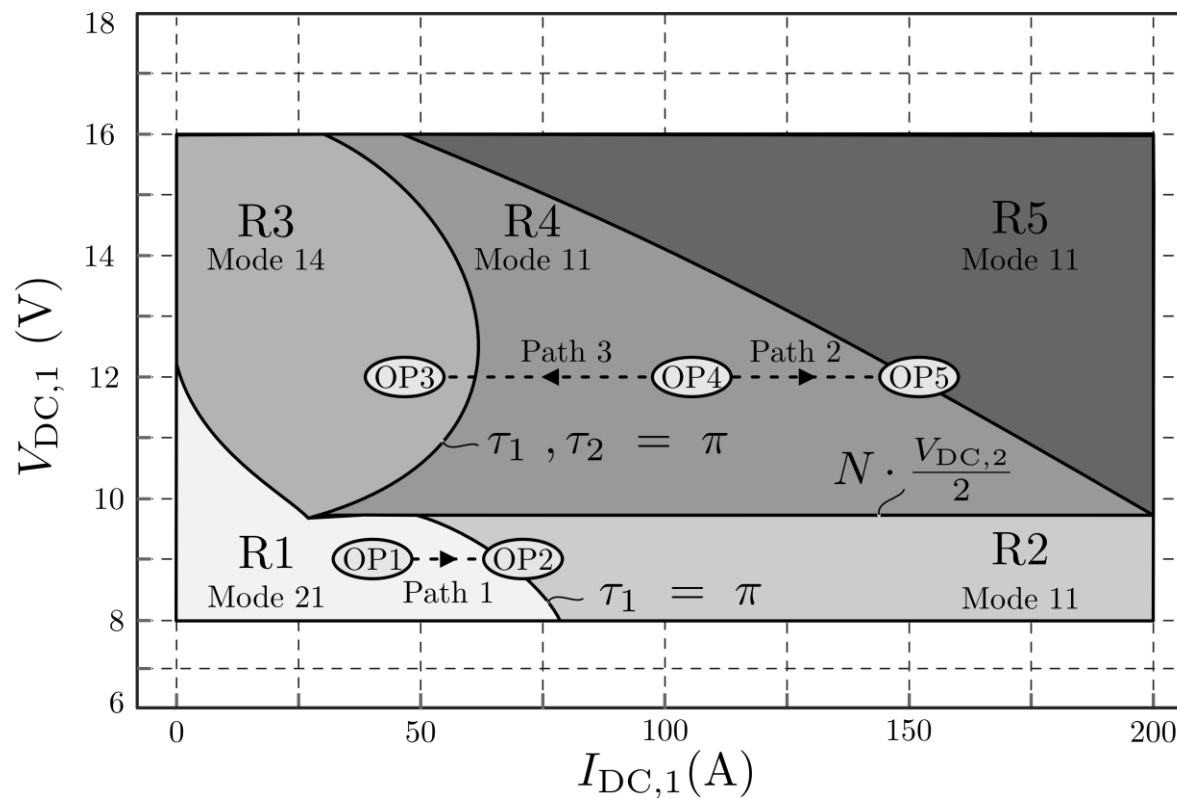


- ZVS achieved in the entire operating region

## LV Bridge


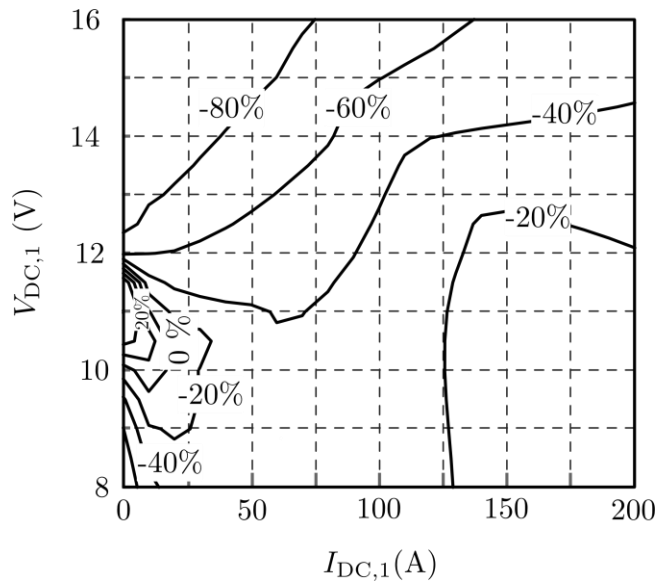


## HV Bridge

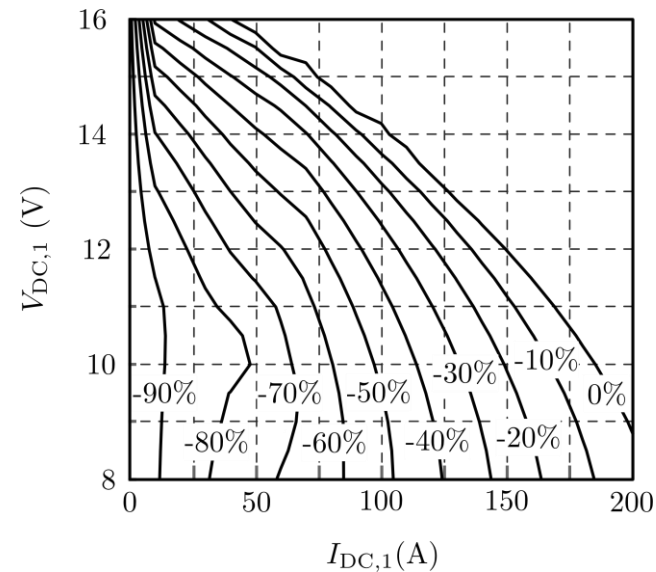

$$RMS\% = 100\% \cdot \frac{I_{RMS,HF_{x,3-5L}}^2(v,i) - I_{RMS,HF_{x,3-3L}}^2(v,i)}{I_{RMS,HF_{x,3-3L}}^2(v,i)}$$


# Experimental Results: Proof of Concept

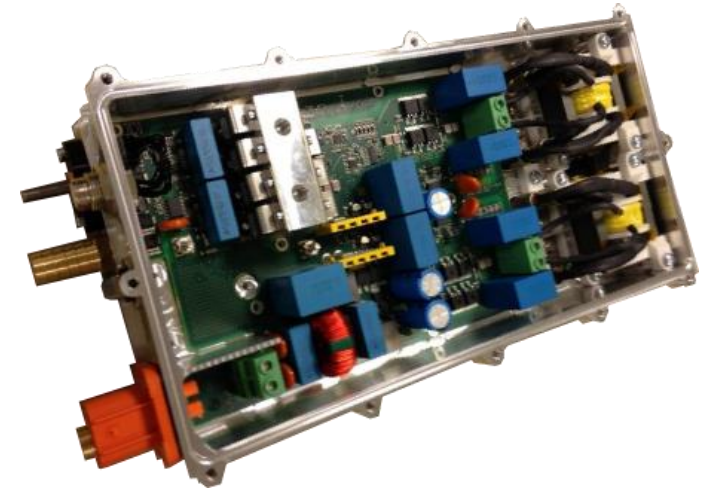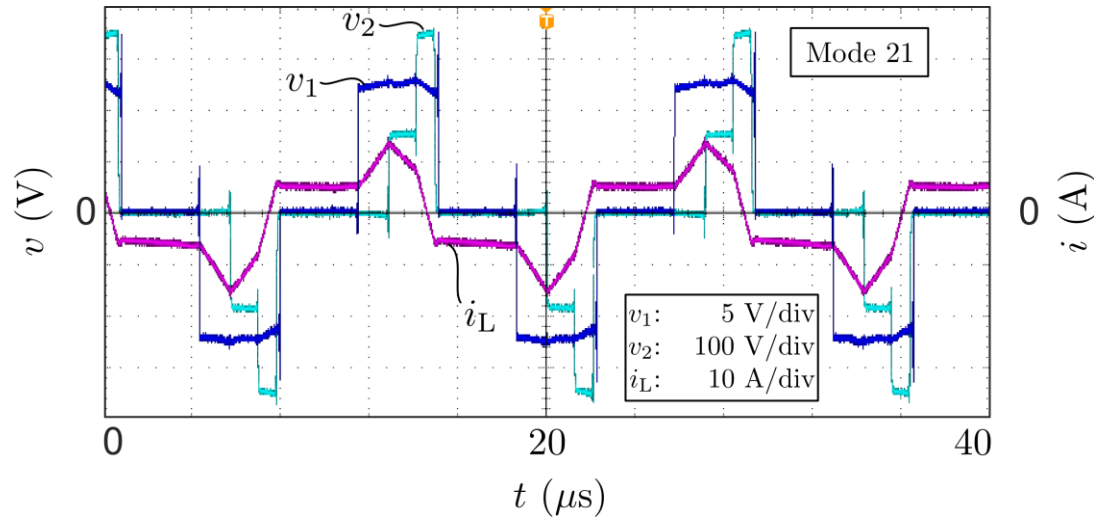


- ▶  $V_{DC,1} = 12 \text{ V}$
- ▶  $V_{DC,2} = 350 \text{ V}$
- ▶  $I_{DC,1} = 32.6 \text{ A}$

Switch (LV)	BUK7Y3R5-40E
Switch (HV)	STW65N65DM2AG
$n_1/n_2 = N$	1/11
$L$	$6.4 \mu\text{H}$
$f_s$	70 kHz

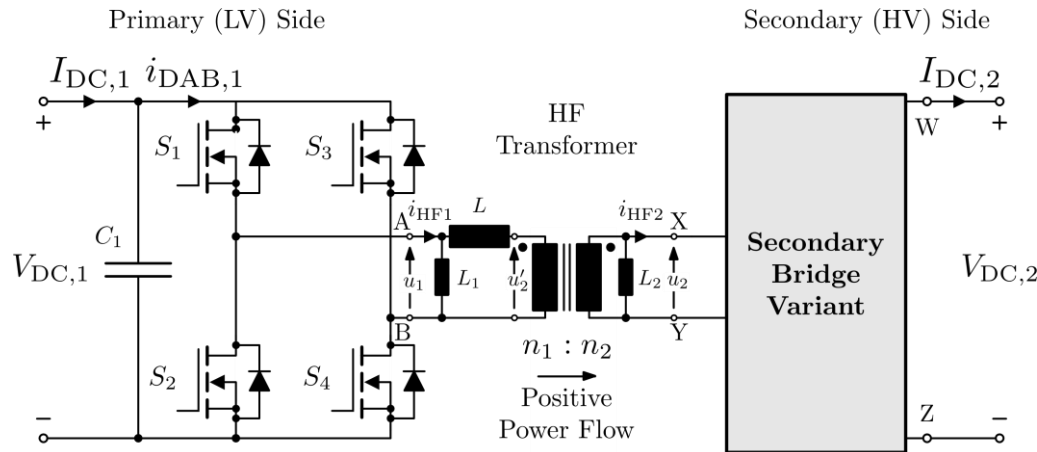
# Comparative Evaluation: Dual Active Bridge Variants




3 Level

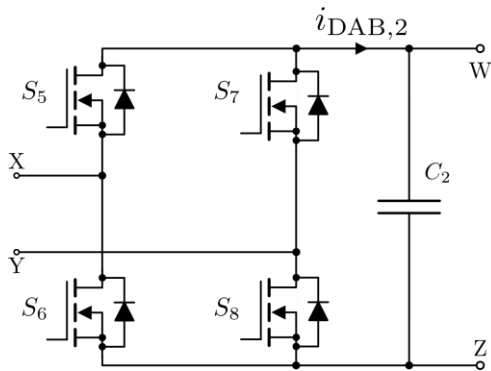






5 Level T-Type

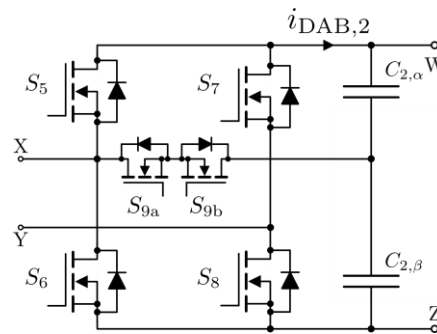

5 Level NPC

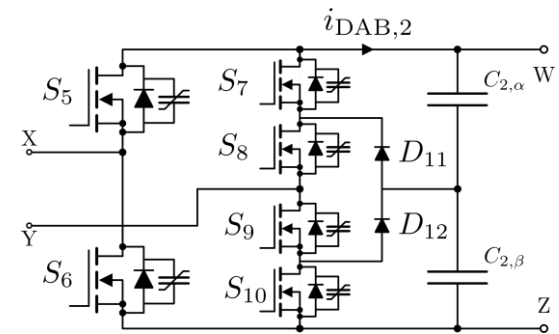

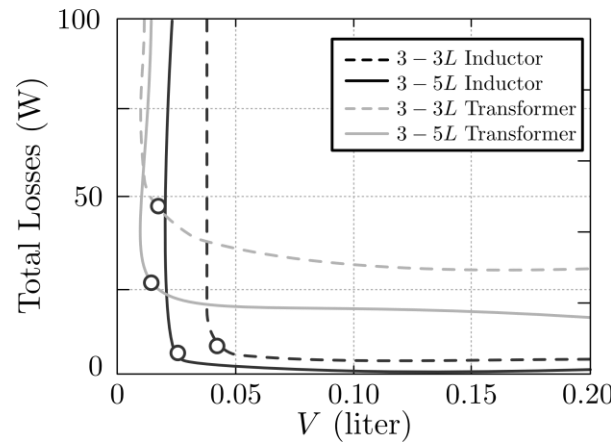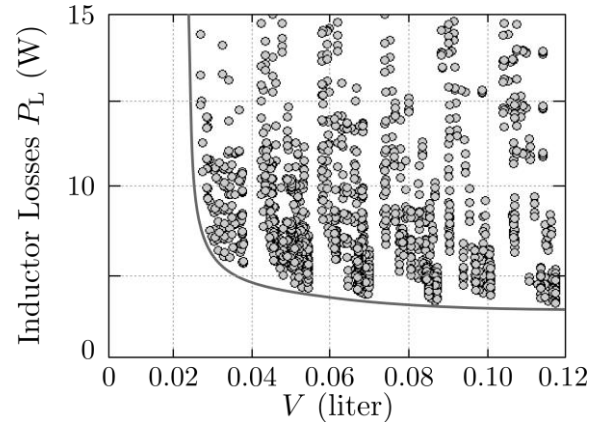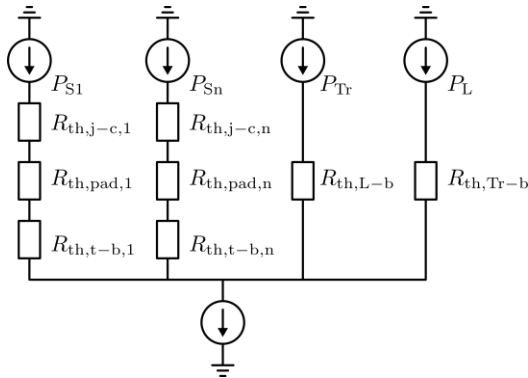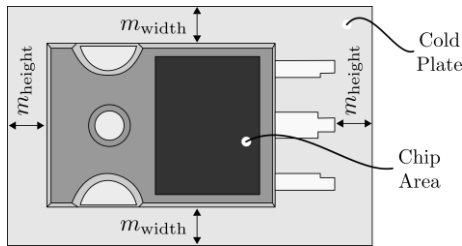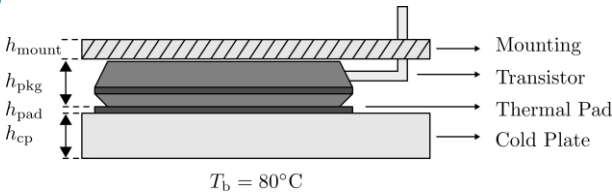
# Comparative Evaluation: Loss and Volume Models




$$Q_x(t) = \int_0^t i_{C_x}(\tau) d\tau$$
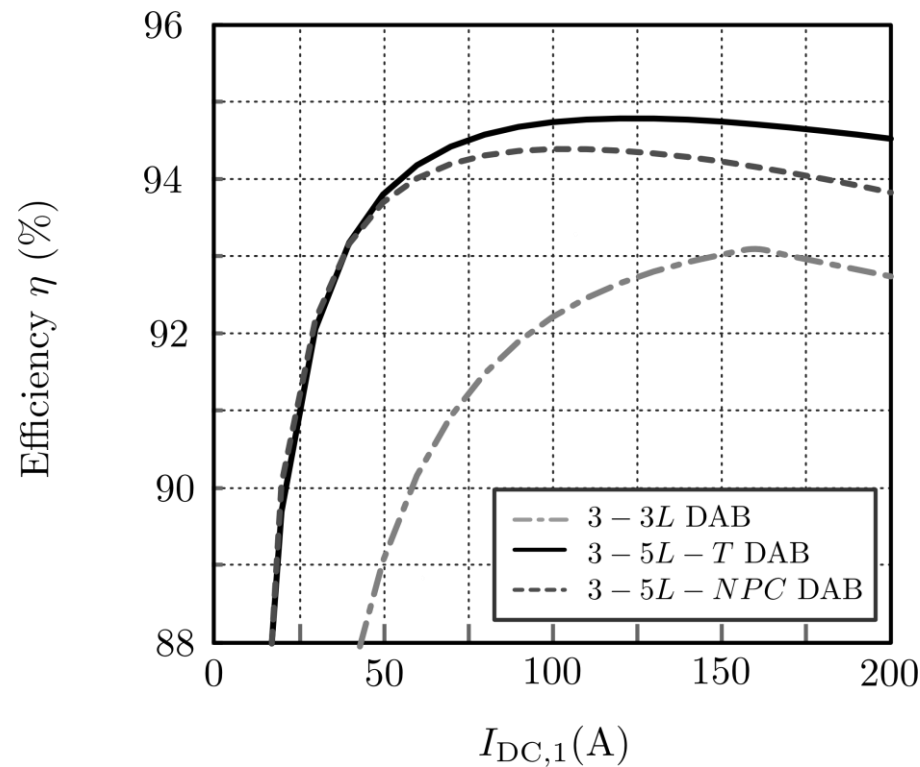
$$C_x = \frac{\Delta Q_x}{V_{DC,x} \cdot f_{ripple}}$$





$$\eta = \frac{P_{DC,in} - (P_S + P_{Magnetics})}{P_{DC,in}}$$
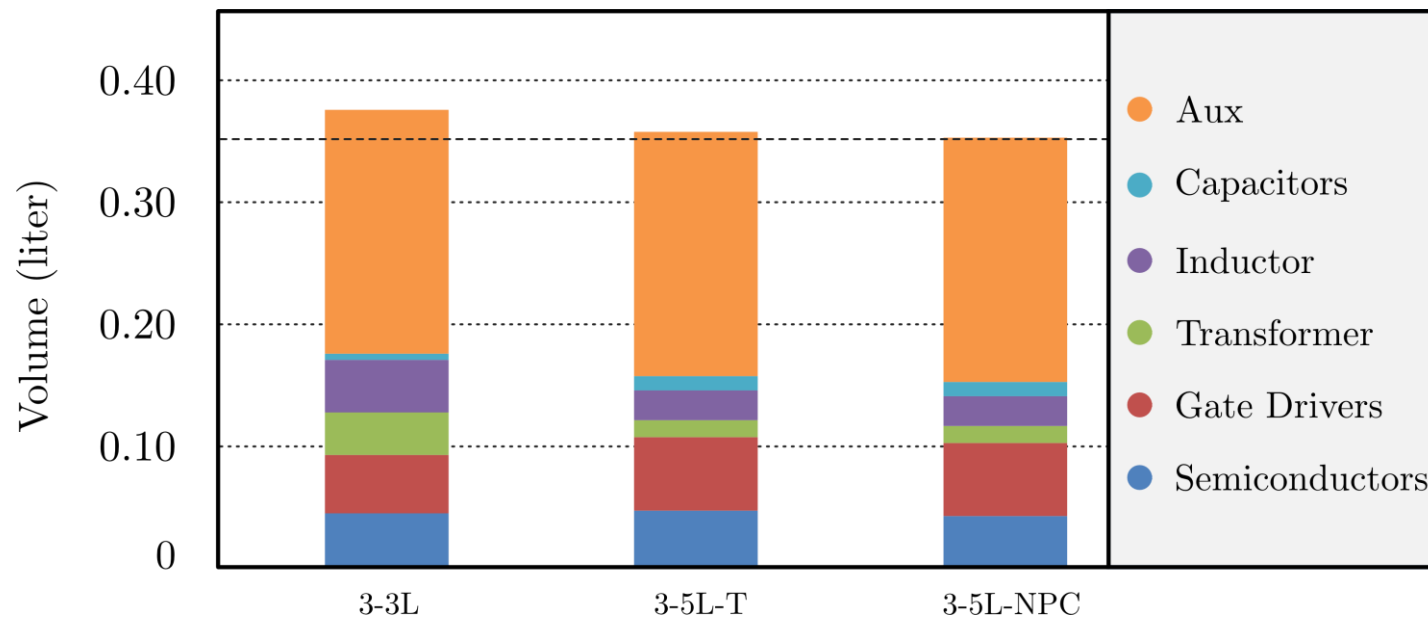
$$\rho = \frac{P_{\text{DC,out}}}{(1 + f_{\text{pack}}) \cdot (V_{\text{sem}} + V_{\text{GD}} + V_{\text{Mag}} + V_{\text{C}} + V_{\text{aux}})}$$



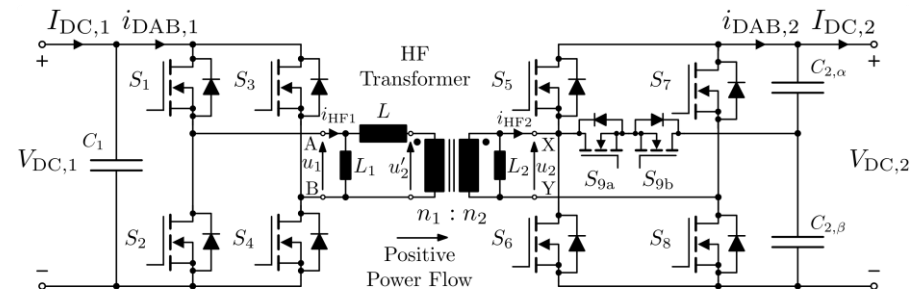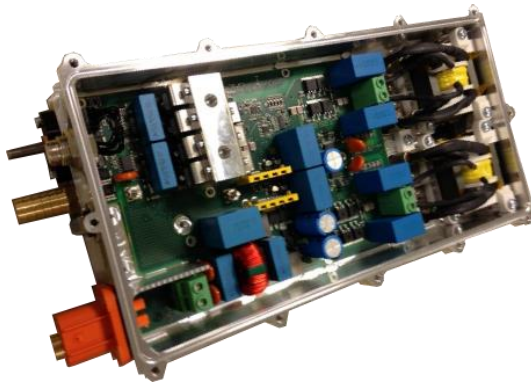- ▶ Multilevel secondary bridge with additional degrees of freedom
- ▶ Analytical charge-based ZVS modulation strategy
- ▶ Comparison of a 3-5L DAB with a 3-3L DAB
- ▶ Experimental verification of the concept
- ▶ Design and realization of an optimized 3-5L DAB DC-DC converter prototype (ongoing)





20 juni 2017  
1931 Congrescentrum Den Bosch

**POWER  
ELECTRONICS** 2017

**Electromechanics and Power Electronics Group**

## **3–5 Level Bidirectional Dual Active Bridge DC–DC Converter**

Thank you for your attention !

**Georgios Sfakianakis, MSc**  
**G.E.Sfakianakis@tue.nl**



**ADEPT**

ADvanced Electric Powertrain Technology

**TU/e**

Technische Universiteit  
**Eindhoven**  
University of Technology

**Where innovation starts**

