



TECHNICAL
ACADEMY

more than you expect





WÜRTH ELEKTRONIK

more than you expect

Reducing inductor size

Alex Snijder
Field Application Engineer

Würth Elektronik



Alex.snijder@we-online.com
+31 6 10 98 48 25


8 OKT ← D&E event 2019

VAN DER VALK HOTEL EINDHOVEN

[illegible]

HOW TO CHOOSE A POWER INDUCTOR



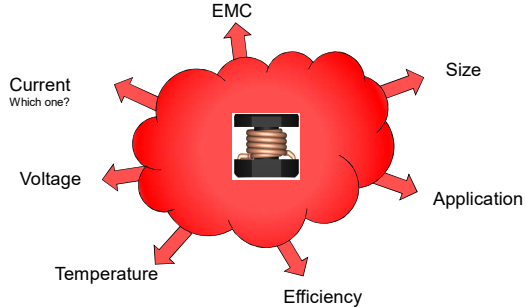

Date 01.03.2016 | Technical Academy | Public/Confidential/ Internal Use | POW_Inductor_Selection


© All rights reserved by Würth Electronics, also in the event of industrial property rights. All rights of disposal such as copying and redistribution rights with us.

www.wi-online.com

3

BUCK CONVERTER : Inductor calculation




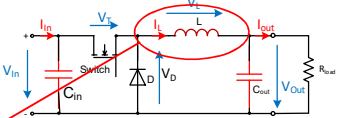


$$L = \frac{(V_{in} - V_{out}) * D}{f_{switch} * r * I_{out}}$$

$r \geq 20\% \text{ and } \leq 40\% \text{ of } I_{out}$

Saturation current

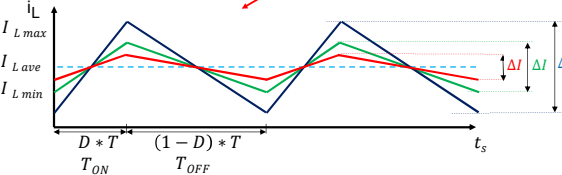

$L \uparrow \Rightarrow r \downarrow$

$L \downarrow \Rightarrow r \uparrow$


Date 01.03.2016 | Technical Academy | Public/Confidential/ Internal Use | POW_Inductor_Selection

© All rights reserved by Würth Electronics, also in the event of industrial property rights. All rights of disposal such as copying and redistribution rights with us.

www.wi-online.com

4

INDUCTOR SELECTION : L vs Current

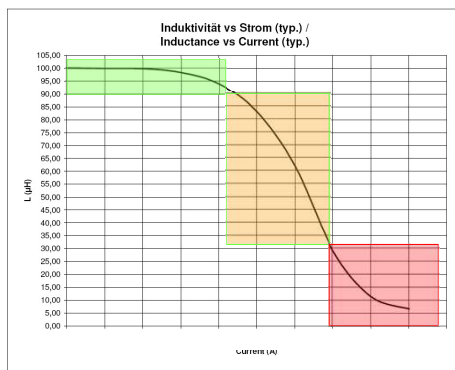

DD.MM.YYYY | Technical Academy | Public | <TITLE>
© All rights reserved by Würth Electronics, also in the event of industrial property rights. All rights of disposal such as copying and redistribution rights with us.

www.we-online.com

INDUCTOR DESIGN : Standard design



Toroidal coil : Iron Powder
WE-SI, WE-FI

Solenoid coil :
NiZn / MnZn
WE-Tix, PD2

Solenoid coil + Shielding
NiZn / MnZn
WE-PD, WE-TPC, WE-PD2SR


Date 01.03.2016 | Technical Academy | Public/ Confidential / Internal Use | POW_Inductor_Selection

© All rights reserved by Würth Electronics, also in the event of industrial property rights. All rights of disposal such as copying and redistribution rights with us.

www.we-online.com

7

INDUCTOR DESIGN : Standard design

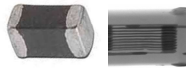

Small size : 0603 to 1210

Multilayer
NiZn and Metal Alloy
WE-PMI, WE-PMCI



Semi Shielded
NiZn
WE-LQS



Plastic Molded
NiZn
WE-GF, WE-GFH

Date 01.03.2016 | Technical Academy | Public/ Confidential / Internal Use | POW_Inductor_Selection
© All rights reserved by Würth Electronics, also in the event of industrial property rights. All rights of disposal such as copying and redistribution rights with us.


www.we-online.com

8

INDUCTOR DESIGN : MOLDED INDUCTOR



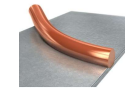Lead frame free-design for
best co-planarity




No solder or welding joints
for highest reliability



Greatest core utilization for highest
current handling



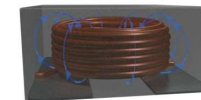Reduce parasitic capacitances
for lowed AC losses



Self shielding construction for
best EMI performance



Protective coating for
perfect robustness

Date 01.03.2016 | Technical Academy | Public/ Confidential / Internal Use | POW_Inductor_Selection
© All rights reserved by Würth Electronics, also in the event of industrial property rights. All rights of disposal such as copying and redistribution rights with us.


www.we-online.com

9

TI-PMLK Buck Würth Elektronik Edition



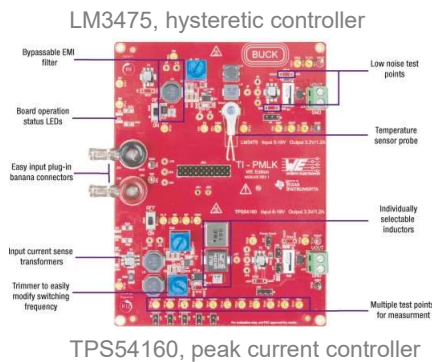- The board allows to analyze:
 - The inherent properties of power inductors, including saturation, losses and thermal effects, and their correlation with physical characteristics
 - The impact of switching regulators operating conditions on the inductors characteristics
 - The impact of inductors characteristics on the operation and performances of switching regulators



© Würth Elektronik 2019 | Technical Academy | Public | <TITLE>


All rights reserved by Würth Elektronik, also in the event of industrial property rights. All rights of disposal such as copying and redistribution rights with us.

www.wk-online.com

Downsizing the inductor, what can we do?



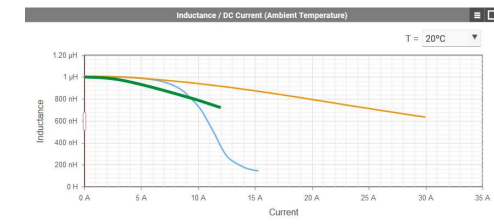- Increase switching frequency
 - Lower inductance
 - Higher core losses in the inductor
 - Lower DC losses in the inductor
 - Higher switching losses MOSFET




- Change core material
 - Optimize core losses in the inductor for higher switching frequencies.
 - Different saturation behavior due to difference in BH-curve and inductor construction.

Order Code	Series	Material	Size	L ₀	R _{DC}	I _{DC}	I _{sat}
74438357010	WE-MAPI	Metal Alloy	4030	1.00 µH	11.6 mΩ	7.40 A	9.60 A
7447779001	WE-PD	NiZn	7345	1.00 µH	10.0 mΩ	5.30 A	9.50 A
74437349010	WE-LHMI	Iron Powder	7050	1.00 µH	6.10 mΩ	10.0 A	19.5 A



© Würth Elektronik 2019 | Technical Academy | Public | <TITLE>

All rights reserved by Würth Elektronik, also in the event of industrial property rights. All rights of disposal such as copying and redistribution rights with us.

www.wk-online.com

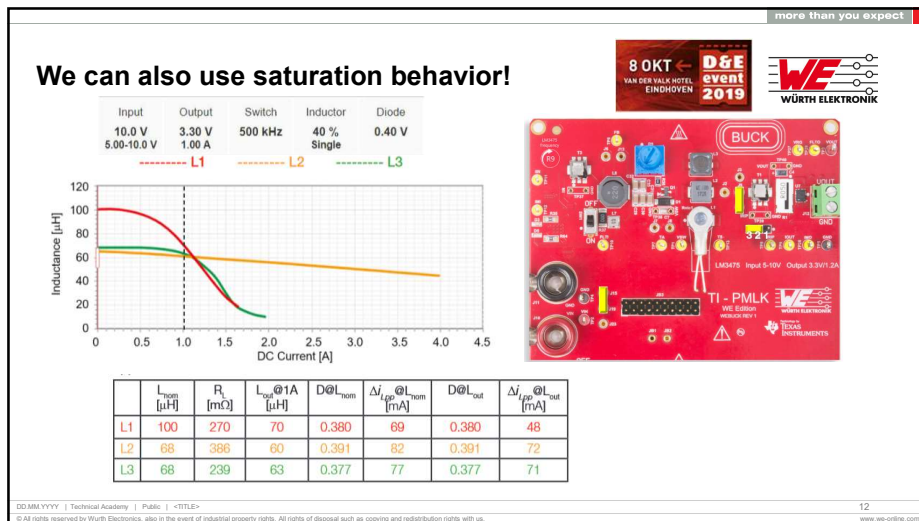

Or use totally different inductors.

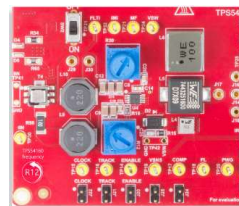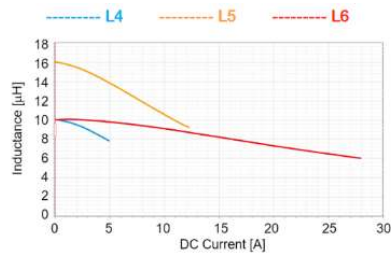

	L	R_L	series	size	core material	length	width	height	vol
	[μH]	[mΩ]				[mm]	[mm]	[mm]	[mm³]
L4	10	101	WE-MAPI	4030	MoL Alloy	4.1	4.1	3.1	52.1
L5	16	34.5	WE-HCI	1050	Superflux	10.5	10.2	5.0	535.5
L6	10	11.4	WE-XHMI	1090	Hyperflux	11.6	10.5	9.1	1108



more than you expect

14

DD.MM.YYYY | Technical Academy | Public | <TITLE>
© All rights reserved by Würth Elektronik, also in the event of industrial property rights. All rights of disposal such as copying and redistribution rights with us.

www.wel-online.com

Compare of L4, L5 and L6

ind.	f_{sw} [kHz]	300		
	I_{out} [mA]	400	800	1200
L4	ΔI_{LSP} [mA]	773	803	815
	$P_{wDC} + P_{wAC}$ [mW] eqs. (11)(12)	23.1	76.3	164.5
	P_{res} [mW] REDEXPERT	31.6	31.0	30.3
	P_{res} [mW]	265.2	530.4	935.6
	η [%]	83.4	83.4	81.1
L5	ΔI_{LSP} [mA]	455	461	466
	$P_{wDC} + P_{wAC}$ [mW] eqs. (11)(12)	6.1	22.7	50.3
	P_{res} [mW] REDEXPERT	17.3	17.1	17.0
	P_{res} [mW]	334.0	690.0	1284.0
	η [%]	85.0	85.0	83.1
L6	ΔI_{LSP} [mA]	805	807	808
	$P_{wDC} + P_{wAC}$ [mW] eqs. (11)(12)	2.4	7.9	17.0
	P_{res} [mW] REDEXPERT	36.3	36.3	36.3
	P_{res} [mW]	265.2	490.4	825.6
	η [%]	83.4	84.5	82.9



- WE-MAPI
- Size 4030
- L = 10uH



- WE-HCI
- Size 1050
- L = 16uH



- WE-XHMI
- Size 1090
- L = 10uH



more than you expect

15



DD.MM.YYYY | Technical Academy | Public | <TITLE>
© All rights reserved by Würth Elektronik, also in the event of industrial property rights. All rights of disposal such as copying and redistribution rights with us.

www.wel-online.com


CCM & DCM

- At low load conditions the converter drops from CCM into DCM or Boundary mode.

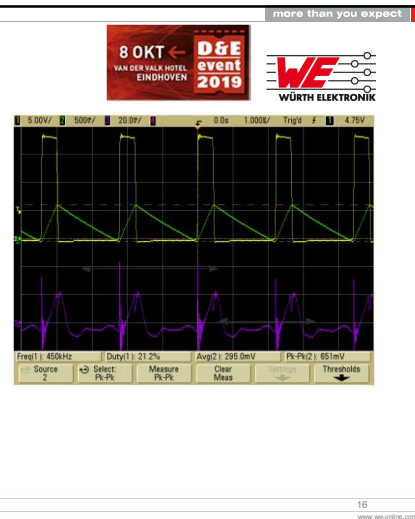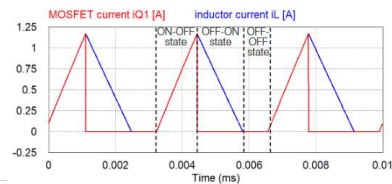- For the inductor this lead to higher peak currents
- Efficient of the convertor will drop
- Not good for EMI
- Ripple voltage on output will increase



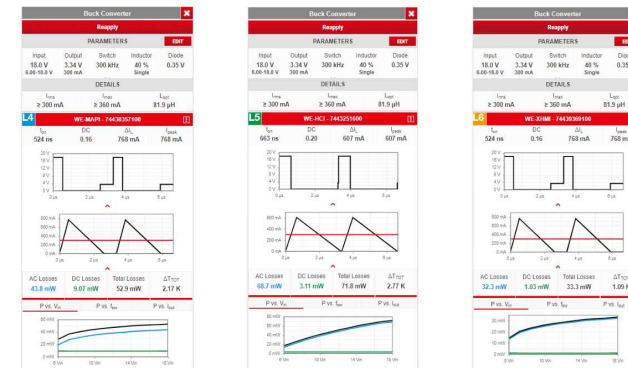RedExpert simulation. 18Vin, 300KHz, 300mA Iout.




we-online.com/redexpert

Summery measurements results



Inductor	L4 (10 µH)		L5 (16 µH)		L6 (10 µH)	
	6	18	6	18	6	18
V_{in} [V]	6	18	6	18	6	18
CCM/DCM operation mode	<input checked="" type="checkbox"/> CCM <input type="checkbox"/> DCM	<input checked="" type="checkbox"/> CCM <input type="checkbox"/> DCM	<input checked="" type="checkbox"/> CCM <input type="checkbox"/> DCM	<input checked="" type="checkbox"/> CCM <input type="checkbox"/> DCM	<input checked="" type="checkbox"/> CCM <input type="checkbox"/> DCM	<input checked="" type="checkbox"/> CCM <input type="checkbox"/> DCM
DC input current I_{in} [mA]	187.1	76.5	184.9	75.8	186.6	76.8
DC output voltage V_{out} [V]	3.337	3.337	3.337	3.337	3.337	3.337
efficiency η [%]	87.7	71.5	88.7	72.2	87.9	71.2
peak-peak inductor ripple current ΔI_{Lpp} [mA]	505	825	295	560	520	830
inductor average current I_L [mA]	295	295	295	295	295	295
peak-peak input ripple current ΔI_{Vpp} [mA]	21	38	20	31	22	44

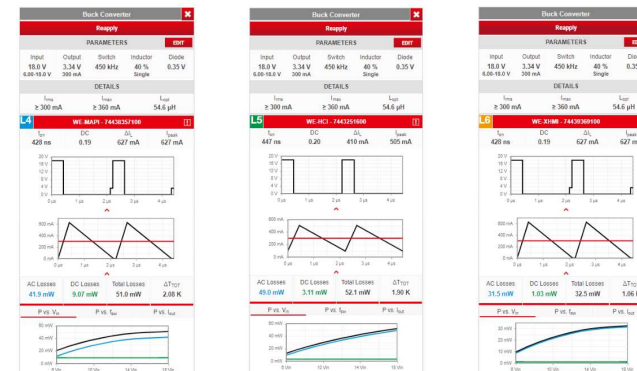RedExpert Simulation 18Vin, 450KHz, 300mA Iout



we-online.com/redexpert

Summery measurements results



fsw = 450 kHz and Iout = 0.3 A

Inductor	L4 (10 µH)		L5 (16 µH)		L6 (10 µH)	
	6	18	6	18	6	18
CCM/DCM operation mode	<input checked="" type="checkbox"/> CCM <input type="checkbox"/> DCM	<input type="checkbox"/> CCM <input checked="" type="checkbox"/> DCM	<input checked="" type="checkbox"/> CCM <input type="checkbox"/> DCM	<input type="checkbox"/> CCM <input checked="" type="checkbox"/> DCM	<input checked="" type="checkbox"/> CCM <input type="checkbox"/> DCM	<input type="checkbox"/> CCM <input checked="" type="checkbox"/> DCM
DC input current I_{in} [mA]	186.9	77.7	185.4	77.5	186.2	77.9
DC output voltage V_{out} [V]	3.337	3.337	3.337	3.337	3.337	3.337
efficiency η [%]	87.8	70.4	88.5	70.6	88.1	70.2
peak-peak inductor ripple current ΔI_{Lpp} [mA]	340	650	200	390	350	665
inductor average current I_L [mA]	295	295	295	295	295	295
peak-peak input ripple current ΔI_{Rpp} [mA]	19	33	17	28	23	38

Hands-on learning kit



- Investigate the impact of magnetics on the performance of a switching power supply
- Help to speed up your design
- Ideal for everyone new in the field of power design but also experienced designers to increase knowledge of magnetic components
- Developed in collaboration with Texas Instruments and with Dr. Nicola Femia, a renowned industry power expert and faculty at the University of Salerno, Italy.
- Get your kit at we-online.com or your local sales contact

Download the experiment book

Complete version - Rev B
The complete version of the PMLK Learning Kit Experiment book

Kit Introduction - Rev B
The Kit introduction and explanation of the board

Experiment 1 - Rev B
Investigate how the inductance of a power inductor changes depending on its physical characteristics and on the operating conditions

Experiment 2 - Rev B
Investigate the impact of inductor power losses on the efficiency of a DC-DC switching regulator

Experiment 3 - Rev B
Analyze the output filtering functions of inductors in DC-DC switching converters

Experiment 4 - Rev B
Analyze the input filtering functions of inductors in DC-DC switching converters

Experiment 5 - Rev B
Analyze the impact of inductors on continuous and discontinuous mode operation of DC-DC switching converters

Experiment 6 - Rev B
Analyze the impact of the inductor on the closed loop load-transient response of a peak-current mode controlled buck regulator

For questions and feedback: pmik@we-online.com

more than you expect

DESIGN AUTOMATION & EMBEDDED SYSTEMS

8 OKT
VAN DER VALK HOTEL
EINDHOVEN
D&E event 2019

WE
WÜRTH ELEKTRONIK

DD.MM.YYYY | Technical Academy | Public | -TITLE-
© All rights reserved by Würth Elektronik, also in the event of industrial property rights. All rights of disposal such as copying and redistribution rights with us.

more than you expect

WE
WÜRTH ELEKTRONIK

Thank you for your attention

more than you expect

DESIGN AUTOMATION & EMBEDDED SYSTEMS

8 OKT
VAN DER VALK HOTEL
EINDHOVEN
D&E event 2019